



SEM 1 – 5 (RC 16-17)

F.E. (Semester – I) (RC 2016 – 17) Examination, May/June 2018 FUNDAMENTALS OF ELECTRICAL ENGINEERING


Duration : 3 Hours

Total Marks : 100


Instructions : 1) Answer **any two** from Part – A and **any two** from Part – B.
2) Answer **any one** from Part – C.

PART – A

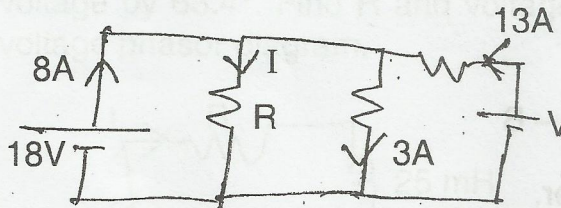
1. a) Explain with neat schematic the working of nuclear power plant. 8
b) What do you mean by mutual inductance ? Derive its expression in terms of related parameters. 6
c) Describe the analogy between an electric circuit and the magnetic circuit. 6
2. a) Find current I and value of resistance R if current distribution in the circuit below is as shown. Also find the value of voltage source V . (2+3+3)



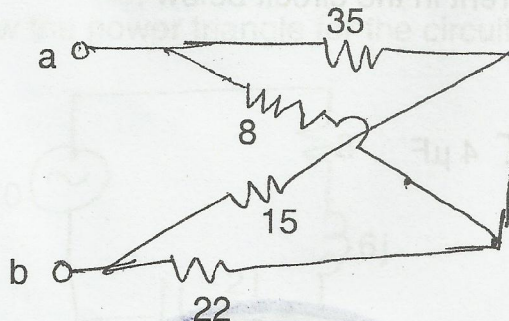- b) In the circuit below find the voltage that should be applied between a and b so that voltage drop of 45 V occurs across 15 Ω resistor. 8




- c) Explain Kirchhoff's laws. 4

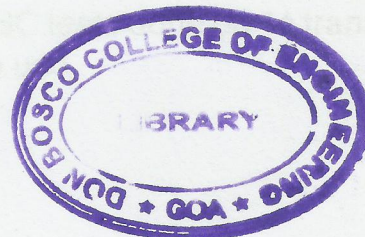


P.T.O.



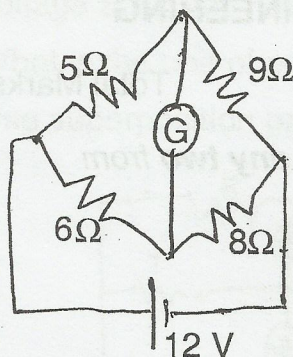3. a) State and explain Thevenin's theorem. 4
- b) Use Norton's theorem to find the current in the galvanometer G, in the Wheatstone's bridge below. The galvanometer resistance $r_g = 2\Omega$. 8





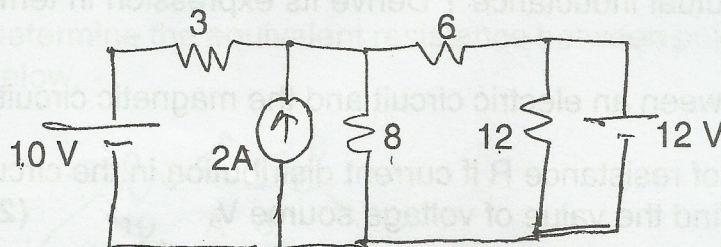- c) Use nodal equations to find all branch current in the circuit below. 8



PART – B

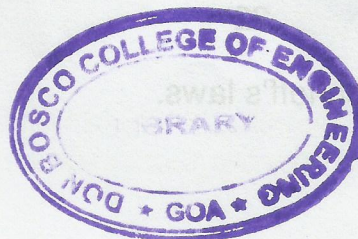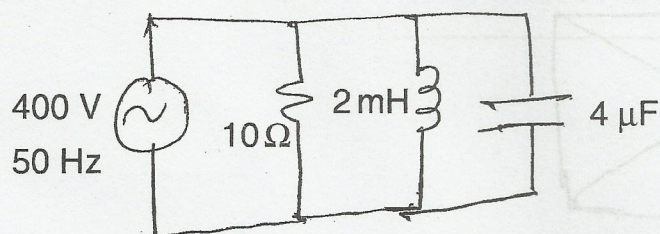4. a) Derive emf equation in 1 ϕ transformer. 4
- b) With the help of neat circuit and phasor diagram show that 3 ϕ power can be measured using two wattmeters. 10
- c) Find branch currents and source current in the circuit below : 6





5. a) What do you mean by :

6


- 1) Lagging and leading power factor
- 2) Phase sequence
- 3) RMS value.

b) A 3ϕ balanced load of $6 + 8j$ is connected in star across balanced 3ϕ 440 V, 50 Hz supply. Find line currents and total power dissipated in the load.

6


c) In the circuit below if the voltmeter reads 45 V across 3Ω , what is the indication on the ammeter ? Also find voltage V.

8

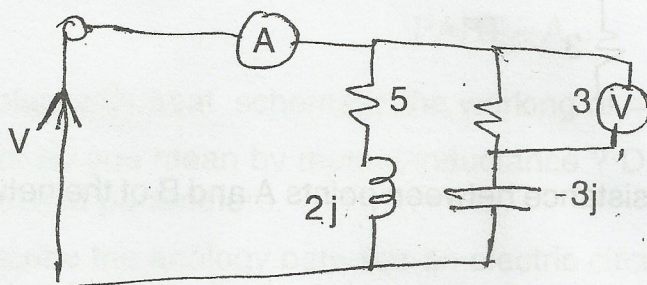


6. a) In the circuit below at frequency $\omega = 400$ rad/sec, the current leads the voltage by 63.4° . Find R and voltage across each circuit element. Draw voltage phasor diagram.

6

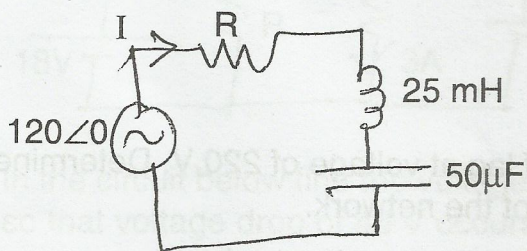


b) Draw the power triangle for the circuit below :

6

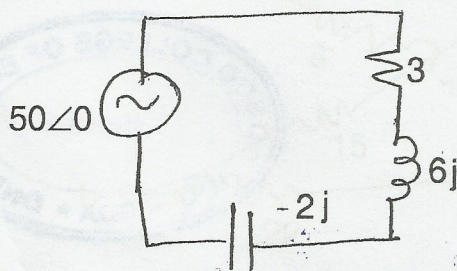

c) With neat circuit diagrams explain OC and SC tests done on 1ϕ transformer. Also explain how the test results are put to use.


8

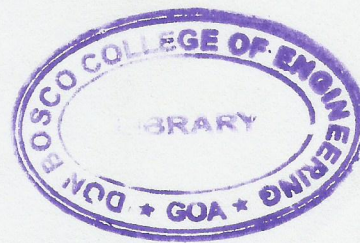




PART – C

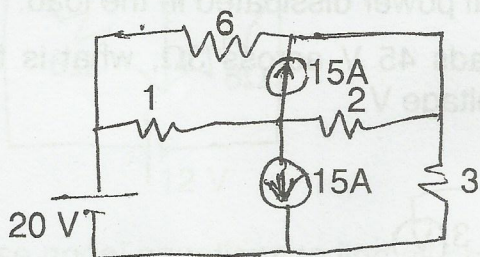7. a) Derive expression for current growth in inductor when it is connected to voltage E through resistor R . 8
- b) What is the unit of power rating of transformer. What it signifies? 4
- c) Use superposition principle to find current in 2Ω resistor in circuit below. 8



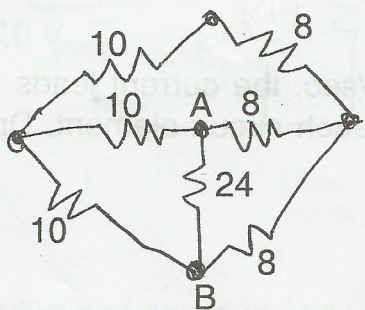8. a) Determine the equivalent resistance between points A and B of the network below. 6



- b) A network draws 10 KW power at 0.8 pf lag at voltage of 220 V. Determine the current drawn and KVAR and KVA of the network. 8
- c) State and prove maximum power transfer theorem for dc circuit. 6

