

**F.E. (Sem. – II) (Revised in 2007-08) Examination, May/June 2008**  
**BASIC ELECTRONIC ENGINEERING**


Duration : 3 Hours

Max. Marks : 100

- Instructions :** 1) Attempt five questions, choosing at least one from each Module.  
 2) Assume any additional data, if necessary.  
 3) Graph papers will be provided on request.

**MODULE – I**

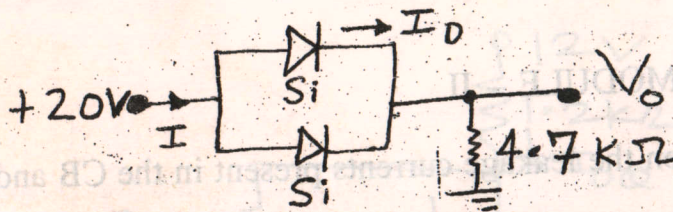1. a) What is a diode and how is the depletion region formed ? 4
- b) Define Knee Voltage, Reverse Saturation Current, Peak Inverse Voltage and Reverse Breakdown Voltage for a diode. 4
- c) Differentiate between Zener and Avalanche breakdowns. 6
- d) With the help of diode circuit and necessary equations, explain how the Q-point is determined. 3
- e) Determine  $I$ ,  $V_0$  and  $I_D$  for the given network. 3



2. a) A bridge rectifier uses load resistor  $R_L = 2K\Omega$ . Each diode has ideal characteristics with slope resistance  $R_f = 10\Omega$ . (Cut-in voltage is assumed to be zero). Input voltage  $V_i$  in each half cycle has amplitude of 20 volts and frequency is 50 Hz. Calculate :
  - i) Peak, dc and rms values of load current
  - ii) DC output voltage and dc output power
  - iii) TuF.6