

Total No. of Printed Pages:04

F.E. (Sem-II) (Revised Course 2016-17)

EXAMINATION Nov/Dec 2019

Fundamentals of Electronics and Telecommunication Engineering

[Duration : Three Hours]

[Total Marks : 100]


**Instructions:**

1. Answer **five** questions. At least two from Part-A, two from Part-B and one from Part-C.
2. Assume suitable data if necessary.
3. Figures to the right indicate full marks.

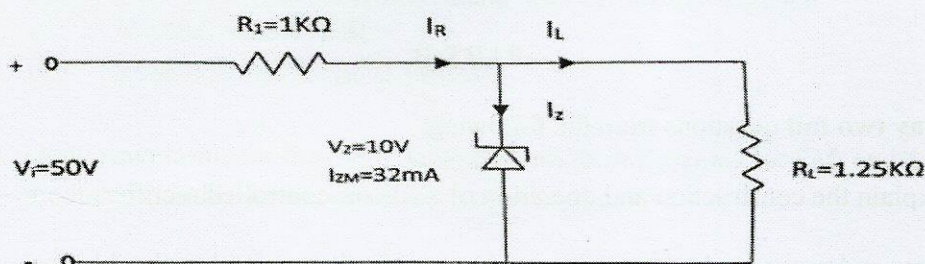**PART- A**

Answer **any two** questions from the following:

- 1
  - a) Draw a reverse biased PN junction diode and explain the following terms: 6
    - i) Reverse Breakdown Voltage
    - ii) PIV of a diode
  - b) With the help of neat diagrams explain the working of a centre-tapped full wave rectifier. Derive the expression for Ripple Factor. 8
  - c) For the network below determine if the Zener Diode is ON or OFF. Find the values of  $V_L$ ,  $V_Z$ ,  $I_L$  and  $P_Z$ . 6




- 2
  - a) Derive the relation between current gain of common-base configuration ( $\alpha_{dc}$ ) and current gain of common-emitter configuration ( $\beta_{dc}$ ) for a transistor. 4
  - b) Explain the input characteristics of an NPN BJT connected in Common Collector configuration with the help of a neat diagram. 5
  - c) What is the need for biasing a transistor? 6





- d) Determine the operating point for the following network.

5

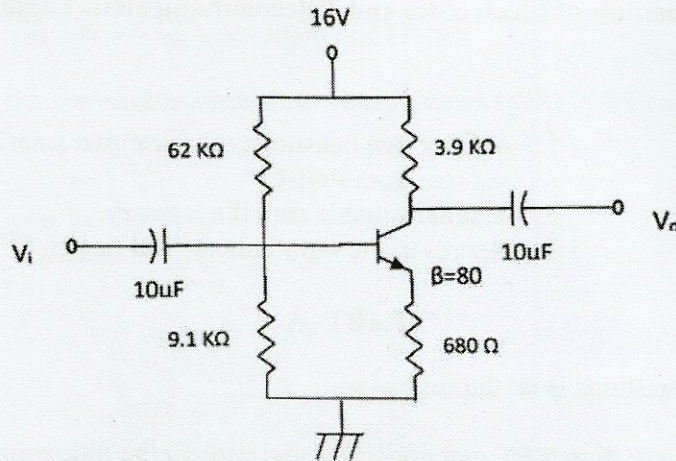

- 3
- Explain the construction and working of a Light Emitting Diode. 7
  - With the help of neat diagrams explain the working of an n-type enhancement MOSFET. 7
  - With the help of a neat diagram explain how CMOS can be used as an Inverter. 6

### PART-B

Answer any two full questions from the following:

- 4
- Explain the construction and operation of a silicon-controlled rectifier. 6
  - State and prove De Morgan's laws using a logic diagram and truth tables. 6
  - Draw the pin diagram of the IC 741 op-amp and explain the function of each pin. Explain the operation for a sinusoid input signal applied to the inverting terminal of an op-amp, and draw the output waveform. 8
- 5
- What is an LVDT? With neat diagrams explain the internal construction and working principle of an LVDT. List two applications. 8
  - Draw the basic block diagram of a PLC and explain its principle of working. 6



- 6
- c) With the help of a neat diagram explain the components of a basic communication system. 6
- a) Why is a NAND gate called a “universal logic gate”? Using logic diagrams, implement the following logic gates using only NAND gates: 6
- i) OR ii) AND
- b) Why is modulation needed in communication systems? With the help of a diagram, explain the basic concept of amplitude modulation. 6
- c) What is a strain gauge? Define “gauge factor” of a strain gauge and write the expression for it. 4
- d) Reduce the following Boolean expression and implement the simplified expression using logic gates: 4
- $$Y = \bar{A}\bar{B} + A\bar{B}$$
- Verify using a truth table.

### PART-C

Answer **any one full** question from the following:

- 7
- a) Explain the limits of operation for a transistor. 5
- b) Simplify the following expression using laws of Boolean algebra: 6
- i)  $Y = ABC + B\bar{C}D + \bar{A}BC$
- ii)  $Y = \bar{A}BC\bar{D} + BC\bar{D} + B\bar{C}\bar{D} + B\bar{C}D$
- c) Draw waveforms for the modulating and modulated signals for FM, and define modulation index for the same. 4
- d) Draw and explain the Ideal Voltage transfer Curve for an Op-amp. 5
- 8
- a) Draw and explain the Drain-Source characteristics of the n-channel JFET. 5
- b) Draw the block diagram of a microcontroller and list two applications. How is it different from a microprocessor? 7
- c) Compare the Common Base, Common Emitter and Common Collector BJT configuration with respect to the following characteristics: 8



- i) Input Resistance
- ii) Output Resistance
- iii) Voltage Gain
- iv) Current Gain
- v) Phase relation between Input and Output

Based on the above characteristics, which configuration is best suited to work as an amplifier?