

## SEM 1 – 4 (RC 07-08)

### F.E. Semester – I (Revised in 2007-08) Examination, May/June 2015 BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours

Total Marks : 100

**Instructions :** 1) Answer **any five** questions with atleast **one** question from **each** module.

2) Assume suitable additional data if **necessary**.

#### MODULE – I

1. a) Define capacitance from its energy and geometrical viewpoints. Derive the expression for equivalent capacitance, when two capacitances are connected in series. 6
- b)  $R_1$ ,  $R_2$  and  $R_3$  are the resistances of the three arms of a star. The star is converted into an equivalent delta, the resistances of which are  $R_a$ ,  $R_b$  and  $R_c$ . Derive the expressions for  $R_a$ ,  $R_b$  and  $R_c$  in terms of  $R_1$ ,  $R_2$  and  $R_3$ . 6
- c) Using Thevenin's theorem, find the current in the  $20\Omega$  resistor for the circuit given in fig (1c). 8

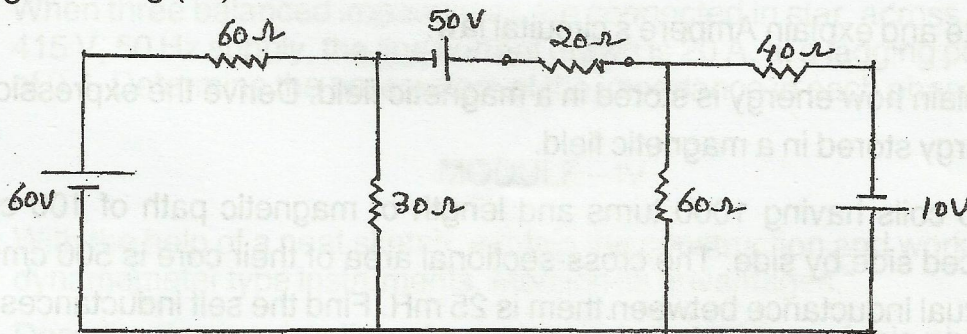


Fig. (1c)

2. a) State and explain Norton's theorem with the help of neat sketches. 6
- b) In the circuit given in fig. (2b), find the value of resistance  $R$  if the current flowing through it is 0.8 Amps. 6

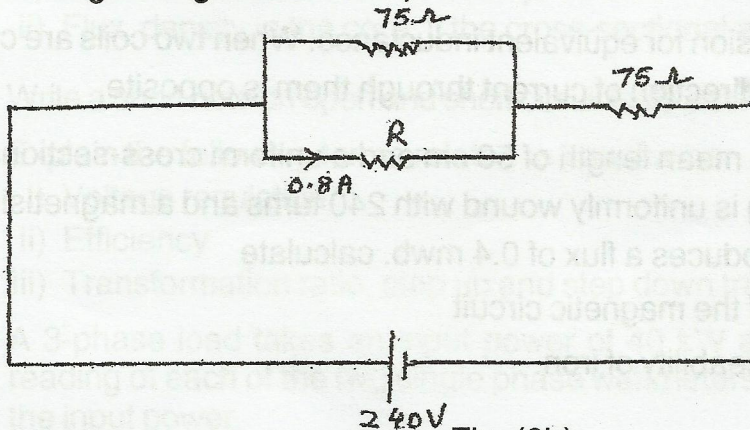


Fig. (2b)

P.T.O.





- c) An inductor of 0.1 H has current waveform as shown in fig. (2c). Sketch the voltage waveform in time synchronism across the inductor.

8


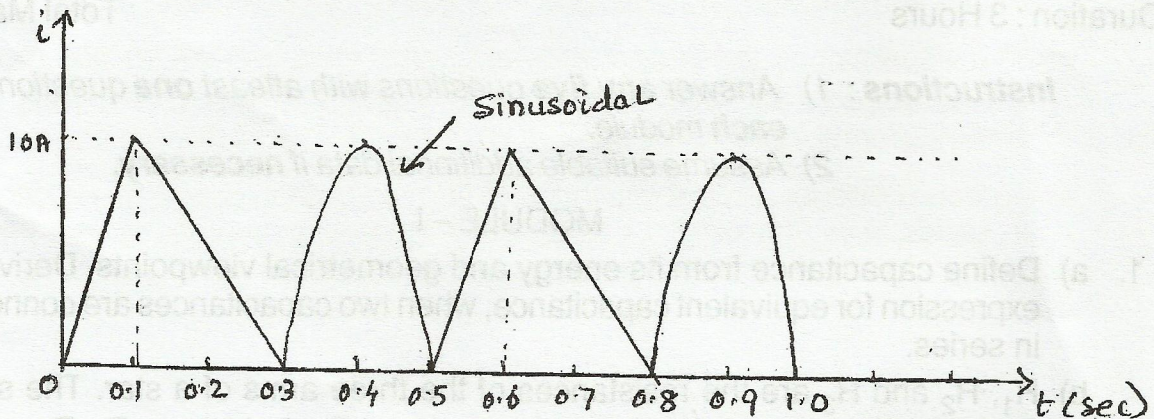


Fig. (2c)

## MODULE – II

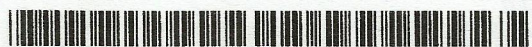3. a) State and explain Ampere's circuital law. 6
- b) Explain how energy is stored in a magnetic field. Derive the expression for energy stored in a magnetic field. 7
- c) Two coils having 1000 turns and length of magnetic path of 100 cm are placed side by side. The cross-sectional area of their core is 500 cm<sup>2</sup>. The mutual inductance between them is 25 mH. Find the self inductances of the coils and the coefficient of coupling between them. What are magnetically coupled coils? 7
4. a) State the similarities and differences between electric and magnetic circuits. 8
- b) Derive the expression for equivalent inductance. When two coils are coupled in series and the direction of current through them is opposite. 6
- c) An iron ring has a mean length of 50 cm and a uniform cross-sectional area of 5 cm<sup>2</sup>. The ring is uniformly wound with 240 turns and a magnetising current of 2A, produces a flux of 0.4 mwb. calculate 6
  - i) Reluctance of the magnetic circuit
  - ii) Relative permeability of iron.





MODULE – III

5. a) Derive the relationships between phase and line currents and also between phase and line voltages in a delta connected balanced three phase system. 8
- b) The expressions for instantaneous values of two currents are given by  $i_1 = 30 \sin(\omega t + 60^\circ)$  and  $i_2 = 10 \sin(\omega t - 45^\circ)$ . Find the expression for the instantaneous value of resultant current by addition of the two currents. 5
- c) A circuit consists of a resistance of  $20 \Omega$ , an inductance of  $0.05 \text{ H}$  connected in series. A supply of  $230 \text{ V}$  at  $50 \text{ Hz}$  is applied across the circuit. Find the current, power factor and power consumed by the circuit. Draw the phasor diagram. 7
6. a) Explain the concept of phasors and show how an ac quantity can be represented by a phasor. 6
- b) Show that, in a single phase c-circuit, the current leads the applied voltage by  $90^\circ$ . Draw the phasor diagram and the waveforms of instantaneous values of voltage and current. 7
- c) When three balanced impedances are connected in star, across a 3-phase,  $415 \text{ V}$ ,  $50 \text{ Hz}$  supply, the line current drawn is  $20 \text{ A}$ , at a lagging power factor of  $0.4$ . Determine the parameters of the impedance in each phase. 7

MODULE – IV

7. a) With the help of a neat sketch, explain the construction and working of dynamometer type instruments. Mention its advantages. 10
- b) Describe the construction of a core type and shell type single phase transformer. 6
- c) The primary winding of a  $25 \text{ KVA}$  transformer has  $200$  turns and is connected to  $230 \text{ V}$ ,  $50 \text{ Hz}$  supply. The secondary turns are  $50$ . Calculate : 4
- i) Full load primary and secondary currents
- ii) Flux density in the core, if the cross-sectional area of the core is  $60 \text{ cm}^2$ .
8. a) Write a short note on open and short circuit tests on a single phase transformer. 8
- b) Explain the following terms related to transformer. 6
- i) Voltage regulation
- ii) Efficiency
- iii) Transformation ratio, step up and step down transformer.
- c) A 3-phase load takes an input power of  $40 \text{ kW}$  at  $0.45 \text{ P.F. lag}$ . Find the reading of each of the two single phase wattmeters connected to measure the input power. 6