

[Total No. of Questions : 8]

F.E. (Semester - I) (Revised in 2007-08) Examination, Nov./Dec. - 2011


BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours


Total Marks : 100

- Instruction : 1) Answer 5 questions in full with at least one question from each module.
2) Missing data, if any, may be suitably assumed.


MODULE - I

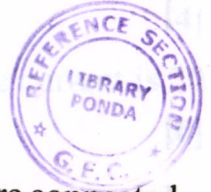

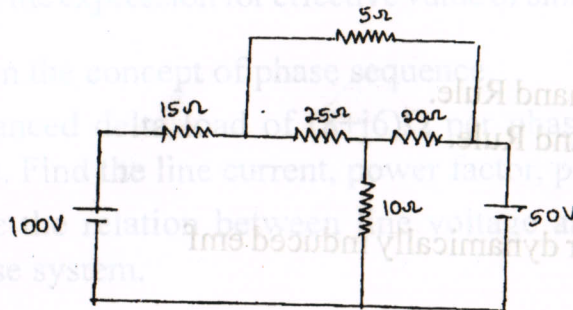
- Q1) a) Derive the equations for equivalent capacitance where four capacitors are connected in series and parallel. [6]
b) Using Kirchhoff's laws find the current in all branches of network shown. [8]



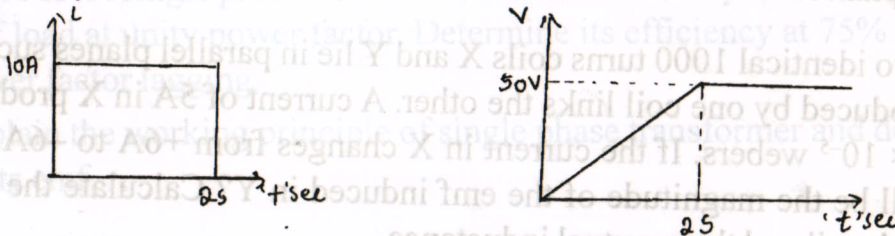
- c) The current and voltage waveforms of an electric device are shown in below fig. Identify the electric device and find out the value of it. [6]



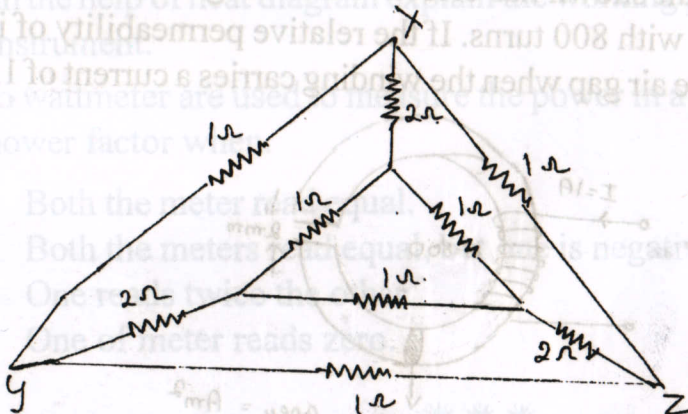- Q2) a) Determine the resistance between X and Y of the network shown in below. State the formulae used. [6]




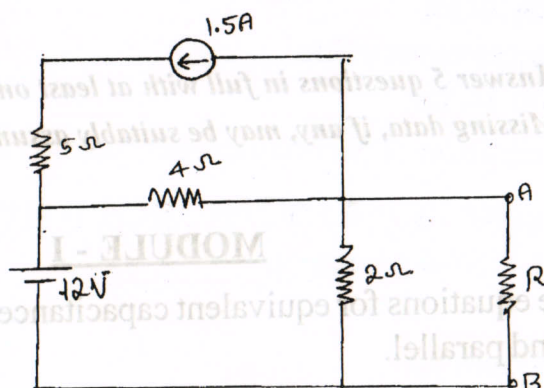- b) State Thevenin's theorem and explain using any circuit. [6]
- c) For the network shown below determine the value of R for maximum power transfer across the terminal A and B and calculate the maximum power that will be delivered to R . [8]



MODULE - II

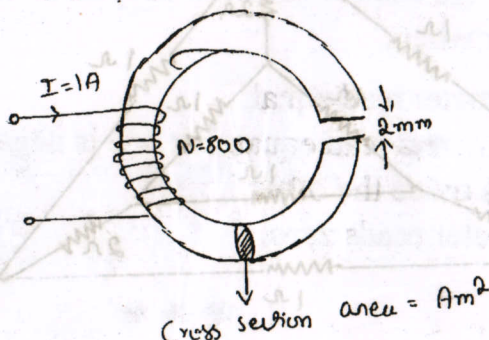- Q3) a) Explain the following : [6]
- Fleming's Right hand Rule.
 - Fleming's Left hand Rule.
 - Lenz's Law.
- b) Derive the equation for dynamically induced emf when [6]
- Conductor moving at right angle to magnetic field.
 - Conductor is moving at an angle θ to the direction of magnetic field.
- c) Explain similarities and dissimilarities between electrical and magnetic circuit. [8]
- Q4) a) Two identical 1000 turns coils X and Y lie in parallel planes such that 60% of flux produced by one coil links the other. A current of 5A in X produces in it a flux of 5×10^{-5} webers. If the current in X changes from +6A to -6A in 0.01 sec. What will be the magnitude of the emf induced in Y? Calculate the self inductance of each coil and their mutual inductance. [7]
- b) Derive the expression for energy stored in a magnetic field. [6]
- c) A magnetic circuit shown has effective iron length of 100 cm and an air gap of 2 mm. It is wound with 800 turns. If the relative permeability of iron 1200. Find the flux density in the air gap when the winding carries a current of 1A (Neglect leakage and fringing). [7]



MODULE - III

- Q5)** a) Define the following : [4]
- RMS value of current.
 - Peak factor.
 - Instantaneous value.
 - Form factor.
- b) Explain addition of two sinusoidal Quantities. [4]
- c) An emf given by $100 \sin(314t - \pi/4)$ is applied to a circuit and the current is $20 \sin(314t - 1.5708)$ Amperes. [6]
- Find :
- Frequency.
 - Circuit element.
- d) Derive the expression for effective value of sinusoidal varying alternating current. [6]
- Q6)** a) Explain the concept of phase sequence. [5]
- b) A balanced delta load of $(8+j6)\Omega$ per phase is supplied from a 3-phase 440v source. Find the line current, power factor, power per phase and total power. [8]
- c) Derive the relation between line voltage and phase voltage in star connected 3-phase system. [7]

MODULE - IV

- Q7)** a) Explain the short circuit test on single phase transformer. [4]
- b) A 600 KVA single phase transformer has an efficiency of 92% both at full load and half load at unity power factor. Determine its efficiency at 75% of full-load at 0.9 power factor lagging. [8]
- c) Explain the working principle of single phase transformer and derive the equation of its emf. [8]
- Q8)** a) Explain the concept of measurement of power in 3-phase circuit using two wattmeter method. [6]
- b) With the help of neat diagram explain the working principle of a dynamometer type of instrument. [6]
- c) Two wattmeter are used to measure the power in a 3-phase balanced system. What is power factor when. [8]
- Both the meter read equal.
 - Both the meters read equal, but one is negative.
 - One reads twice the other.
 - One of meter reads zero.

