



F.E. (Semester – I) (R.C. 2007-08) Examination, November/December 2012
BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer 5 questions in **full**, with atleast **one** question from **each** Module.
2) Missing data, if any may be **suitably** assumed.

MODULE – I

1. a) Derive the expression for equivalent capacitance, when two capacitances are connected in :

6

- i) Series and
- ii) Parallel.

- b) Using Thevenin's theorem, find the current flowing in the $10\ \Omega$ resistor.

7

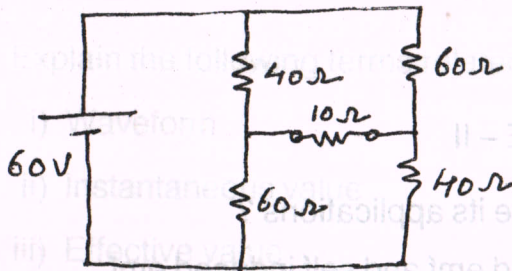


Figure (1b)

- c) Calculate the current supplied by the source, in the series-parallel circuit shown. Also find the voltage drops across the $2\ \Omega$ resistances.

7

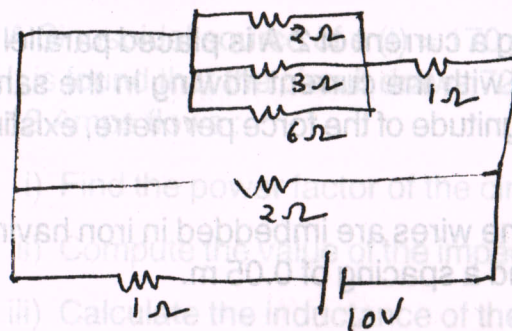


Figure (1c)

P.T.O.



2. a) State and explain Norton's theorem. 6
- b) Calculate the resistance of 100 m length of wire having a uniform cross-sectional area of 0.1 mm^2 , if the wire is made of manganin having resistivity of $50 \times 10^{-8} \Omega - \text{m}^2$. If the wire is drawn out to three times its original length, by how many times would its resistance increase ? 6
- c) Using mesh analysis, determine the current in the 1Ω resistance in the circuit as shown in fig. (2c). 8

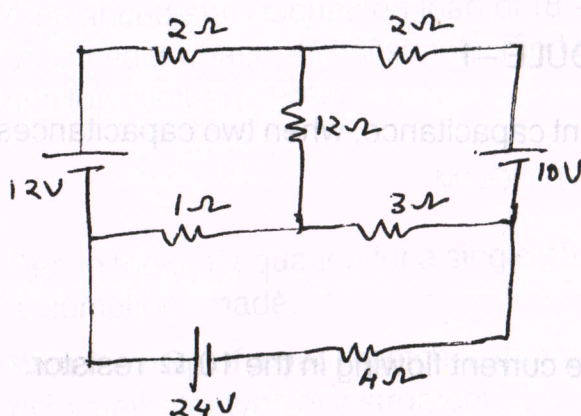


Figure (2c)

MODULE – II

3. a) State and explain Lenz's Law. What are its applications ? 6
- b) Explain the concept of mutually induced emf and self induced emf. 7
- c) A long straight wire located in air carries a current of 4A. Assume the relative permeability of air is unity :
- i) Find the value of the magnetic field intensity at a distance of 0.5 m from the centre of the wire.
 - ii) A second long straight wire carrying a current of 2 A is placed parallel to the first one at a distance of 0.5 m with the current flowing in the same direction. Find the direction and magnitude of the force per metre, existing between the wires.
 - iii) Repeat part (ii) for the case when the wires are imbedded in iron having a relative permeability of 10,000 and a spacing of 0.05 m. 7



4. a) Derive the expression for magnetic field strength at a distance r , for a long straight current carrying conductor. Hence derive expression for flux density. 6
- b) Distinguish between : 7
- i) Mutually induced emf and self induced emf.
 - ii) Statically induced emf and dynamically induced emf.
- c) The total inductance of two coils A and B when connected in series is 0.5 H or 0.2 H depending on the relative directions of the current in the coils. Coil A when isolated from coil B, has a self inductance of 0.2 H. Calculate : 7
- i) The mutual inductance between the two coils
 - ii) The self inductance of coil B
 - iii) The coupling factor between the coils
 - iv) The two possible values of the induced emf in coil A, when the current is decreasing at 1000 A/S in the series circuit.

MODULE – III

5. a) Explain the following terms related to ac quantities : 5
- i) Waveform
 - ii) Instantaneous value
 - iii) Effective value
 - iv) Frequency
 - v) Cycle.
- b) Derive the relationship between phase and line quantities in a delta connected three phase system. 8
- c) A Sinusoidal source of $e(t) = 170 \sin 377t$ is applied to an RL series circuit. It is found that the circuit draws 720 w power, when an effective current of 12 Amps flows : 7
- i) Find the power factor of the circuit.
 - ii) Compute the value of the impedance.
 - iii) Calculate the inductance of the circuit in Henrys.



6. a) With a neat sketch explain how an alternating voltage is produced, when a coil is rotated in a magnetic field. Derive an expression for the instantaneous value of alternating sinusoidal emf in terms of its maximum value, angular frequency and time. 7
- b) Derive a relationship between current and voltage in a pure inductive and in a pure capacitive circuit. Draw the waveforms of instantaneous values of voltage and current. 7
- c) A balanced star connected load of $(8 + j6) \Omega$ per phase is connected to a balanced 3-phase, 400 V supply. Find the line current, power factor, power and total volt-amperes. 6

MODULE – IV

7. a) Derive the emf equation for a single phase transformer. Mention the assumptions made. 6
- b) With the help of a neat sketch, explain the construction and working of dynamometer type of instrument. 9
- c) A single phase, 50 Hz transformer is required to step down from 1900 V to 240 V. It is to have 1.5 V per turn. Calculate the required number of turns on primary and secondary windings respectively. The peak value of the flux density is required to be not more than 1.2 wb/m^2 . Calculate the required cross-sectional area of the steel core. If the output is 10 KVA, calculate the secondary current. 5
8. a) Explain the two Wattmeter method of measurement of power in a three- phase circuit. 6
- b) Write a short note on the following : 8
- i) Rating of a single phase transformer
- ii) Losses in a single phase transformer.
- c) With the help of a neat phasor diagram, explain the working of single phase transformer on no load. 6