

Total No. of Printed Pages:04

**F.E. Semester-II (Revised Course 2007-08)**  
**EXAMINATION Aug/Sept 2019**  
**Basic Electronic Engineering**

[Duration : Three Hours]

[Max. Marks : 100]


**Instructions:**

1. Attempt any five questions choosing at least one question from each module.
2. Assume suitable data only if necessary.


**Module I**

Q.1

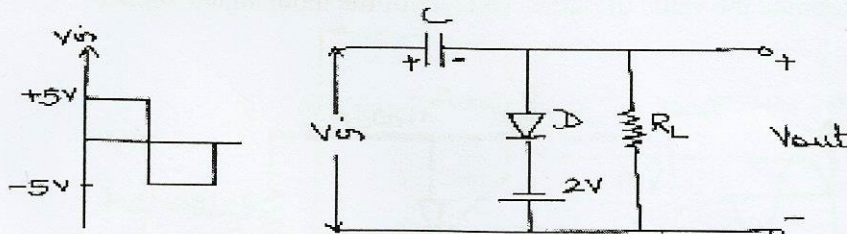- a) Sketch the output waveform of the circuit shown in fig. It is given that the discharging time constant is greater than the time period of input wave. (5)



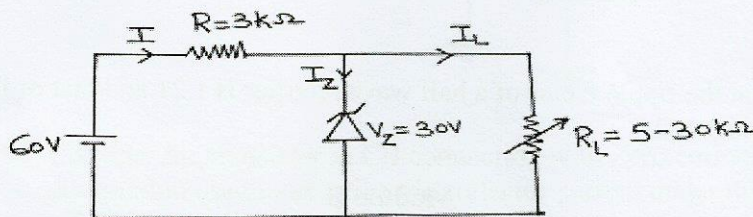
- b) Using Ideal Zener diode approximations. Find current through the diode of fig when load resistance R is i)  $30K\Omega$  ii)  $5K\Omega$  (8)



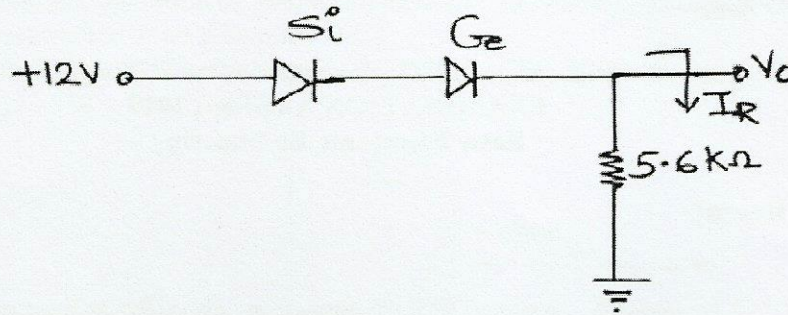
- c) Explain the effect of temperature on V-I characteristics of diode. (4)  
 d) Determine  $V_O$ ,  $I_D$  for the network. (3)







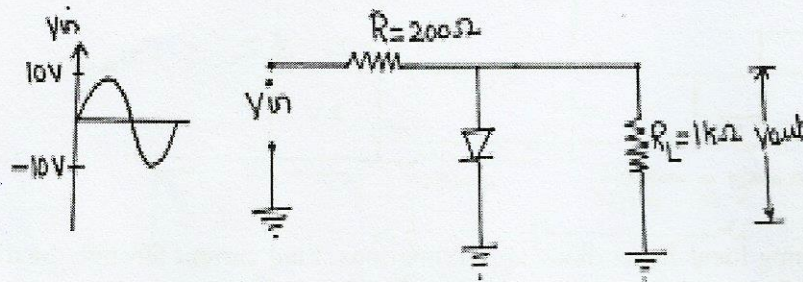- Q.2
- a) In a center tapped Full wave rectifier, the rms half secondary voltage is 10v. Assuming ideal diodes and load resistance of  $R_L = 2K\Omega$ . Find the following (5)
- Peak current
  - Dc voltage
  - Ripple factor
  - Efficiency of Rectification
- b) Determine the value of output voltage for the input signal applied. (5)




- c) Prove that the ripple factor of a half wave rectifier is 1.21 and that of full wave rectifier is 0.482. (10)

### Module II

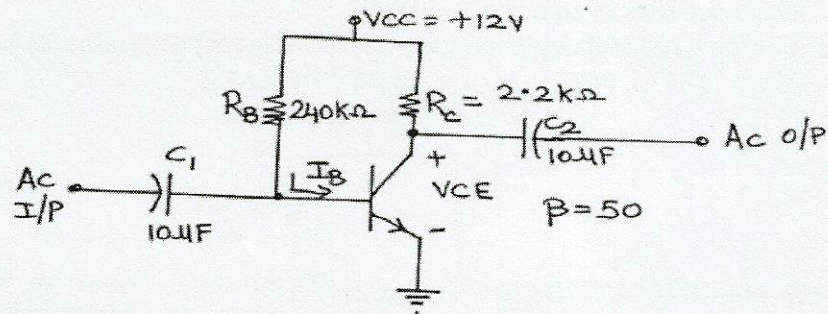- Q.3
- Explain how a transistor can be used as an amplifier. (4)
  - Draw and explain the input and output characteristics of common Emitter (CE) Configuration. (7)
  - Determine the following for the fixed bias configuration of the fig given below (6)
    - $I_{BQ}$  and  $I_{CQ}$
    - $V_{CEQ}$
    - $V_B$  and  $V_C$
    - $V_{BC}$






d) What is Thermal Runaway and how it can be controlled. (3)

Q.4

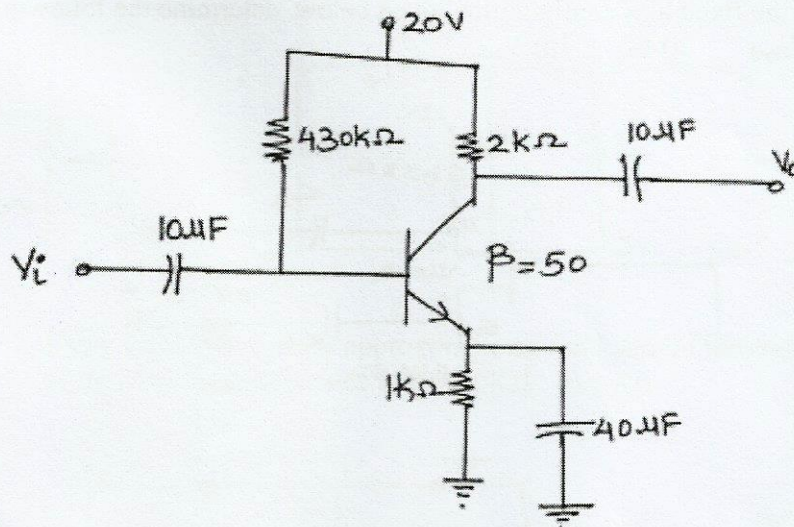a) For the Emitter bias Network Determine  $I_B$ ,  $I_C$ ,  $V_{CE}$ ,  $V_C$ ,  $V_E$ ,  $V_B$  and  $V_{BC}$ . (7)



b) Consider the transistor in CB connection with Zero emitter current. What is the designation used to describe the collector current under this condition. What effect would a reduction in temperature have on this current. (6)

c) Distinguish between the emitter, base and collector regions of a transistor. (7)  
Derive the relationship between the current gains of CB and CE transistors.

### Module III

Q.5


a) Explain with the help of a constructional diagram the working of a CMOS Inverter. (5)

b) Explain the working of n channel depletion type MOSFET. Also Draw the output and transfer characteristics for N channel depletion type MOSFET. (10)


c) Explain why JFET is called a voltage controlled resistor. (5)



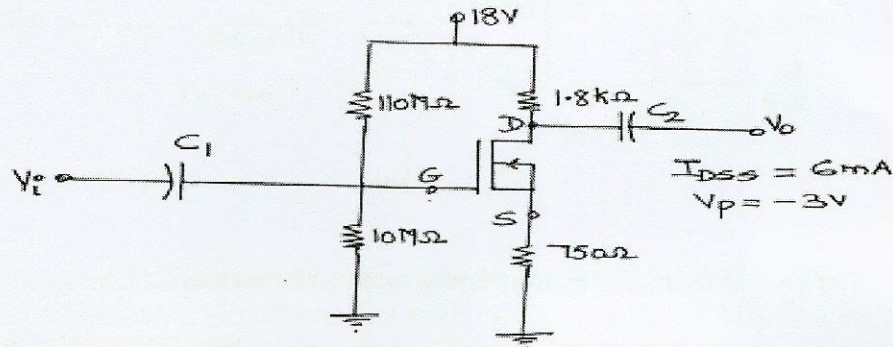- Q.6
- Explain the operation of an n channel JFET. Also Draw the output and transfer characteristics of an n channel JFET. (8)
  - For the n channel depletion type MOSFET of fig determine a)  $I_{DQ}$  and  $V_{GSQ}$  b)  $V_{DS}$  (6)



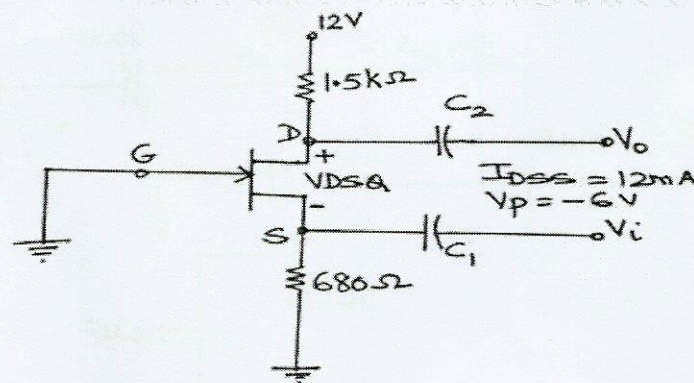- For the fixed bias configuration given below, determine the following: (6)
  - $V_{GSQ}$
  - $I_{DQ}$
  - $V_{DS}$



#### Module IV

- Draw and explain Internal Block diagram of OP-AMP. (6)
  - Explain the working of SCR using two transistor equivalent circuits. (6)
  - Write a note on Photodiode. (4)
  - Explain the manufacturing steps involved in fabrication of discrete diode. (4)
- Explain the basic diagram of CRT. (6)
  - Write a note on Thermistor. (4)
  - Draw the block diagram of the feedback circuit used as an oscillator. Explain Barkhausen Criterion for oscillation. (6)
  - Explain the working of Reflective type field effect LCD. (4)