

Total No. of Printed Pages:4

**F.E. Semester-II (Revised Course 2007-08)
EXAMINATION OCTOBER 2020
Basic Electronics Engineering**


[Duration : Two Hours]

[Total Marks :60]

- Instructions:-** 1) Answer THREE FULL QUESTIONS with ONE QUESTION from ANY THREE MODULES.
2) Make suitable assumption, if required.


Module – I

 - Q1. a) Explain the formation of the depletion region in a pn diode. (4)
- b) Plot the V – D characteristics of a pn junction diode and define static resistance from the curve. How does reverse saturation current vary with temperature? (5)
- c) Briefly explain the concept of transition and diffusion capacitances associated with pn diode and draw the relevant graph illustrating how these capacitances vary with the applied bias. (6)
- d) Discuss the Zener breakdown mechanism. What is the effect of increased temperature on Zener breakdown voltage? (5)
- Q2 a) Determine the current I for the given configuration. (2)




- 2 b) A voltage $v=7.1 \sin \omega t$ is applied across each half of the secondary winding of a centre tapped full wave rectifier. Assuming ideal diodes, if the resistance of the half secondary winding is 1.5Ω and the load resistance is $1K\Omega$, determine: (4)
- i) DC voltage
- ii) Peak and DC current
- iii) DC power delivered to the load.
- 2 c) Discuss the effect of resistance and capacitance values chosen on the output waveform of a C-filter. (2)

 - 2 d) For the given zener diode network, find V_L , V_R and I_Z (3)



- 2 e) Draw and explain the circuit of a negative clipper with output waveform. (2)

 - 2 f) Determine the output waveform for the following clamper circuit assuming ideal diode and large RC time constant. (4)




- 2 g) Draw the circuit diagram and waveforms of a halfwave Voltage Doubler (3)

Module – II

 - Q3 a) When the emitter current of a transistor is changed by 1mA, its collector current changes by 0.995 mA. Calculate
 i) Its common base current gain α
 ii) Its common emitter current gain β . (4)
- 3 b) Draw the laboratory (circuit) setup of a CB pnp transistor and explain how the static output characteristics are plotted. Find the output resistance from the curves. (8)
- 3 c) Explain how a CE transistor can be used as an amplifier. (6)
- 3 d) Identify and label the limits of operation on the output characteristics of a CE amplifier (2)

- 4 a) Find the Q-point (I_{CQ} and V_{CEQ}) for the give si transistor where $\beta = 100$ (6)



- 4 b) What is the need for bias stabilization? Define Stability Factor S. Which bias circuit has the highest 'S' factor? Derive it. (8)


- 4 c) With the help of a sketch, define the time intervals of a pulse waveform encountered in a switching transistor. (6)

Module – III

- Q5. a) With the help of a neat diagram, explain the operation of a n- channel JFET. Show the internal depletion region and explain their shapes. (8)

 
- b) For fixed bias Configuration given below. Determine V_{DS} , V_{GG} and V_{GSQ} by using graphical approach:

Given: $V_D = 9V$, $I_{DSS} = 8mA$, $V_P = -4V$



- c) Explain why JFET is called a voltage controlled device? A p-Channel JFET has device parameter of $I_{DSS} = 6mA$ and $V_P = +6V$ and $V_P = +6V$. Sketch transfer characteristics. (5)

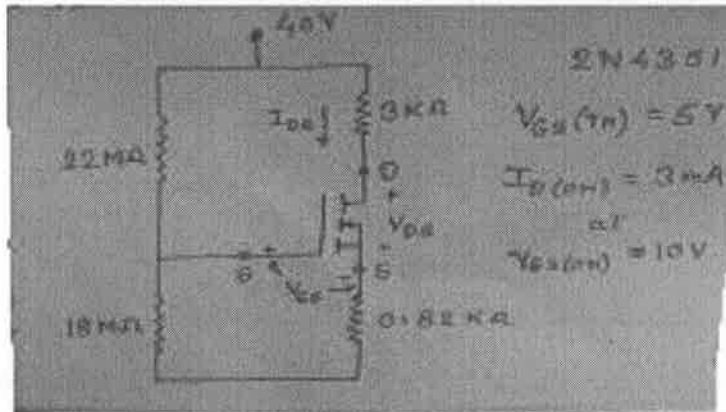- Q6. a) Determine I_{DQ} , V_{GSQ} and V_{DS} for the Circuit shown below: (8)



- b) Differentiate between the following:
 i) BJT and JFET
 ii) DMOSFET and EMOSFET (4)
- c) If gate to source voltage is n-channel DMOSFET is made more positive, does drain Current increase beyond I_{DSS} or it decrease? Justify your answer with reason. (4)
- d) Explain with the help of a diagram the basic CMOS operation. (4)

Module – IV

- Q7. a) Explain various steps involved in fabrication of Monolithic ICs. (10)
- b) Draw and explain the internal block diagram of OPAMP. (6)
- c) Explain Nyquist criterion. What is its significance? (4)
- Q8. a) Explain dark current with respect to photodiode. (4)
- b) Explain the application of photo conductive cell in a voltage regulator. (5)
- c) Describe the behaviour of SCR using the 2 transistor equivalent circuit. (6)
- d) How is internal synchronization is achieved in CRO? (5)