

Total No. of Printed Pages:3

F.E. Semester-II (Revised Course 2007-2008)
EXAMINATION Nov/Dec 2019
Basic Electronic Engineering

[Duration : Three Hours]

[Total Marks : 100]

Instructions:

1. Attempt any five questions choosing at least one question from each module.
2. Assume suitable data only if necessary


Module I

Q.1

- a) Define and explain static and average resistance of a diode with the help of a diagram. (4)
- b) Draw and explain center tapped full wave Rectifier circuit and derive the expression for ratio of (10)
rectification
- c) What is an ideal diode? Sketch the characteristics of an ideal diode. (6)


Q.2

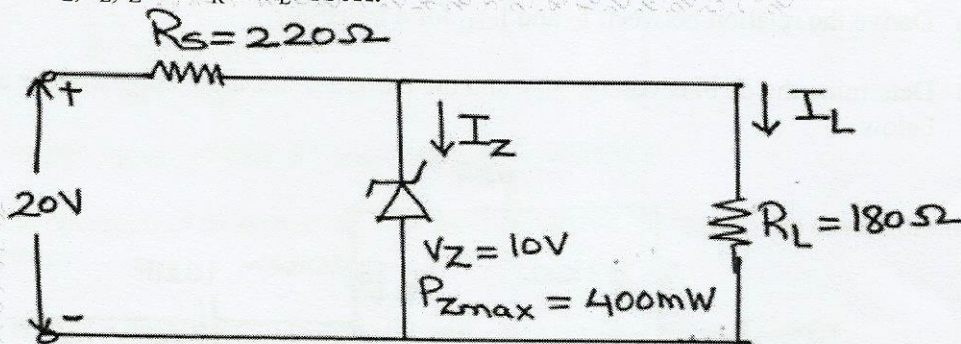- a) Determine V_L , I_L , I_Z and I_R if $R_L = 180\Omega$. (4)




- b) Why is a filter required in a dc power supply? Draw the circuit of a C filter and explain the output waveform (6)

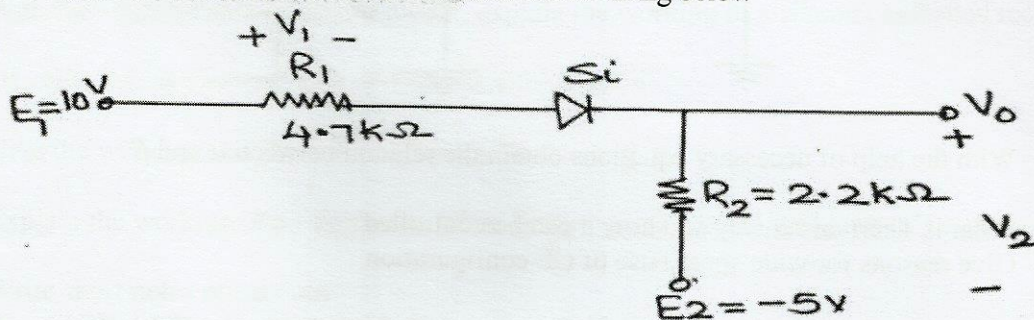- c) Determine I , V_1 , V_2 and V_o for the network shown in fig below (5)




- d) What is the peak output voltage of the circuit in fig below (5)



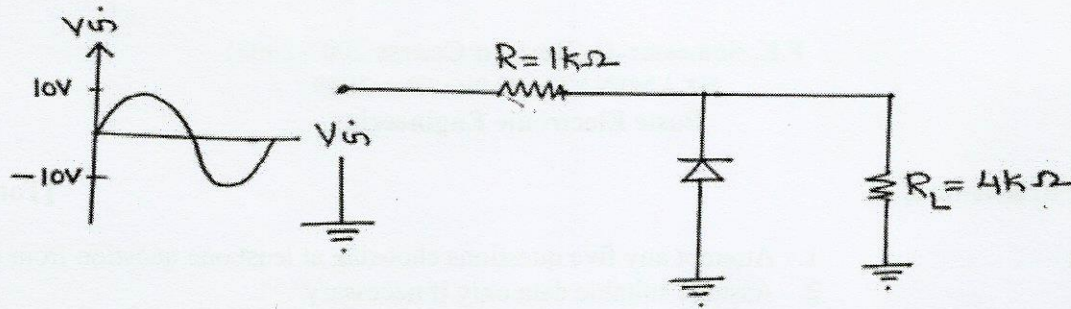

Module II

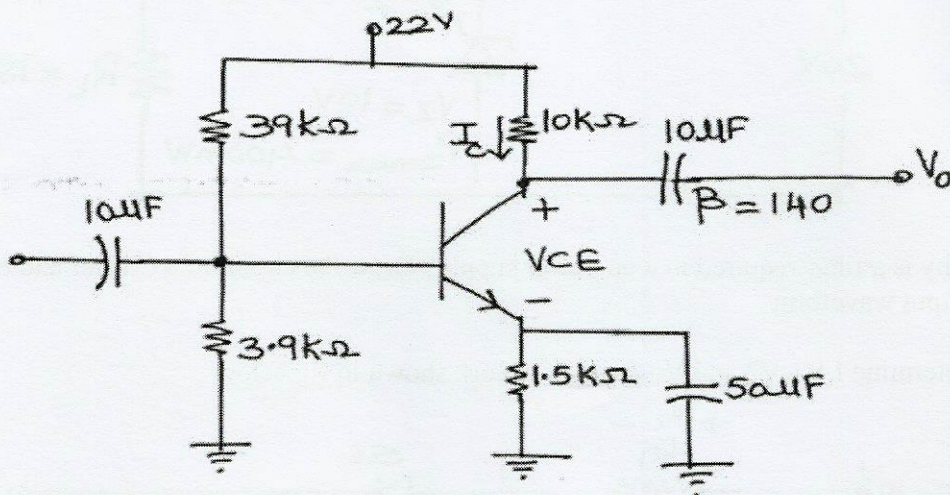- Q.3
- Compare the Biasing methods. Which is the best biasing technique? Explain any one biasing technique. (6)
 - Explain how Transistor can be used as an amplifier (5)
 - Explain CE configuration of an NPN transistor. Draw the input and output characteristics (6)
 - Derive the relation between I_C and I_{CEO} for a transistor (3)
- Q.4
- Determine the dc bias voltage V_{CE} and the current I_C for the voltage divider configuration of fig below (8)




- With the help of necessary equations obtain the relation between α and β . (4)
- What is Thermal runaway and how it can be controlled (4)
- Give reasons for wide spread use of CE configuration (4)

MODULE III

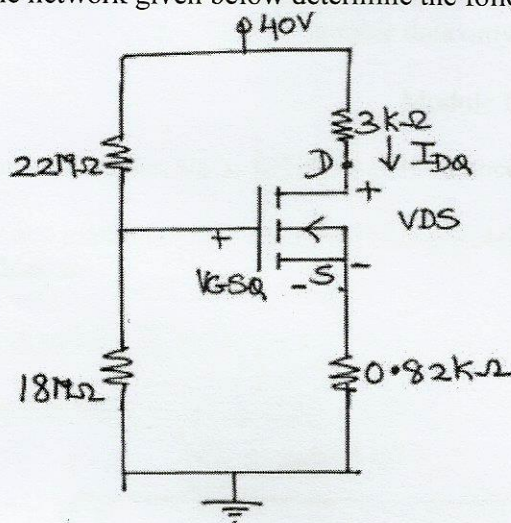Q.5

- With the help of neat diagram explain how Complementary MOSFET can be used as an Inverter (6)
- Explain the working of a n-channel JFET. Draw the transfer characteristics and output characteristics. (8)
- For the network given below determine the following i) V_{GSQ} ii) I_{DQ} iii) V_{DS} (6)



$$\begin{aligned} V_{GS}(Th) &= 5V \\ I_D(on) &= 3mA \\ V_{GS}(on) &= 10V \end{aligned}$$

Q.6

- Explain the biasing circuit of an Enhancement mode MOSFET. (6)
- Explain the operation of an n-channel depletion type MOSFET. Sketch the device drain characteristics (8)
- With the help of a neat diagram explain the self-bias configuration of a JFET (6)

Module IV

Q.7

- Explain the working and use of solar cell (6)
- With the help of a two transistor model, explain the working of a silicon controlled rectifier (6)
- Describe the various methods of Transistor fabrication (8)

Q.8

- Give the working and characteristics of SCR. (8)
- Explain the working of an oscillator. What is the significance of Barkhausen's criteria? (8)
- Write short notes on any one (4)
 - OP-AMP
 - Photoconductive cell
 - IR Emitter