

Total No. of Printed Pages:3

F.E. Semester- II (Revised Course 2016-17)

EXAMINATION AUGUST 2021

Fundamentals Of Electronics And Telecommunication Engineering

[Duration : Two Hours]


[Total Marks : 60]

Instructions:


- 1) Answer THREE FULL QUESTIONS with ONE QUESTION FROM EACH PART.
- 2) Assume suitable data if necessary.
- 3) Figures to right indicate full marks.

PART – A

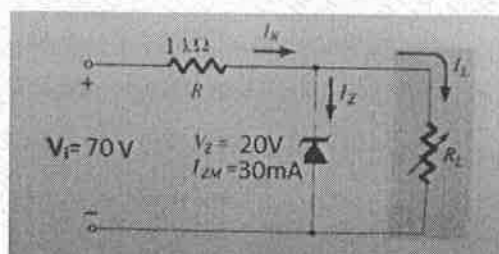- Q.1
- a) With the help of neat sketch explain reverse biasing of PN junction diode. 5
 - b) Draw the V/I characteristic of Ge diode and explain the term threshold or knee voltage. 5
 - c) Differentiate between half wave rectifier and a center-tapped full wave rectifier. 5
 - d) For the network shown below, determine the range of R_L and I_L that will result in V_{R_L} being maintained at 20 V. 5



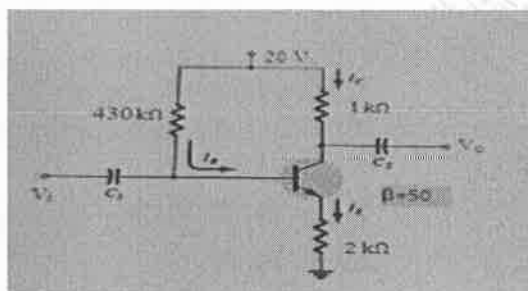- Q.2
- a) Drive the relation between leakage currents of CB (I_{CBO}) and CE (I_{CEO}) configuration. A certain transistor has α_{dc} of 0.98 and a collector leakage current I_{CO} of $1\mu A$. Calculate the collector and the base currents, when $I_E = 1mA$. 5
 - b) With the help of a neat circuit diagram explain the output characteristics of a npn BJT connected in common Emitter (CE) configuration. 5
 - c) What is a biasing circuit and what are the requirements from a biasing circuit? 5
 - d) For the emitter-bias network shown below, determine : 5
 - i) I_B
 - ii) I_C
 - iii) V_{CE}
 - iv) V_C
 - v) V_{BC}



- Q.3
- Derive an expression for the rectification efficiency of a full wave bridge rectifier. 5
 - Explain different types of atomic bonds. 5
 - With the help of a neat diagram explain the construction of P-channel JFET. 5
 - What are the various ways in which transfer characteristics of a JEFT can be plotted? 5


PART – B

- Q.4
- Draw the pin configuration of IC 741, and explain the use of each pin. 5
 - With the help of neat diagram, explain the circuit of a inverting amplifier using opamp and give the expression of its closed loop voltage Gain. 5
 - State the associative Law of Boolean Algebra and prove it using the truth Table method 5
 - Draw the symbol of SCR and with the help of a neat diagram explain the construction of Silicon Controlled Rectifier. 5
- Q.5
- With the help of neat sketches explain the construction, working and characteristics of light dependent resistor (LDR). Also give an application of LDR. 5
 - With the help of neat block diagram explain the components of PLC. 5
 - What is printed circuit board? What are the advantages of having a PCB over point to point soldered circuit? 5
 - With the help of waveforms, explain the basic concept of amplitude modulation. 5
- Q.6
- Two square waves, A of 1 KHz and B of 2 KHz frequency are applied as input to the following logic gates. Draw the output waveform in each case. 5
 - NAND Gate
 - XOR Gate

- b) With respect to op-amp explain the term common mode rejection Ratio. Also explain what is the need of feedback in an op-amp? 5
- c) Explain the working principle of piezoresistive gauges. 5
- d) With the help of a flowchart give the steps involved in design and fabrication of single sided PCB. 5

PART – C

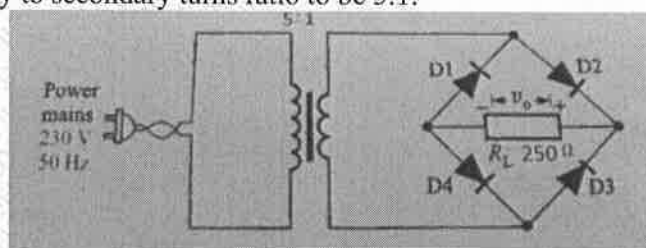- Q.7
- a) A crystal diode having internal resistance $r_d = 20$ is used for half wave rectification. If the applied voltage $v = 50 \sin \omega t$ and load resistance $R_L = 800$ ohms find:
i) I_m, I_{dc} ii) A.C. power input and D.C. power output iii) D.C. output voltage 5
- b) With the help of neat diagram explain how complementary MOSFET (CMOS) can be used as an inverter. 5
- c) With the help of neat diagram explain the characteristics of an SCR. 5
- d) What is a programmable Logic Controller? 5
- Q.8
- a) In the bridge rectifier circuit shown in figure below, the diodes are assumed to be ideal find :
i) The d.c. output voltage
ii) The peak inverse voltage
iii) The output frequency
iv) Ripple factor
Assume primary to secondary turns ratio to be 5:1. 5



- b) Differentiate between emitter, base and collector region of transistor. 5
- c) With the help of logic diagrams, explain NOR gate is called as an Universal Gate. 5
- d) Explain the following steps involved in the manufacturing of a single –sided printed circuit Board : 5
i) Artwork Generation
ii) Panel preparation

