

Total No. of Printed Pages: 3

F.E. Semester-I (Revised Course 2007-2008)
EXAMINATION MAY/JUNE 2019
Basic Electrical Engineering

[Duration : 3 Hours]


[Max. Marks : 100]

Instruction:-


- 1) Answer any five questions with atleast one question from each module.
- 2) Assume suitable additional data if necessary.

Module - I

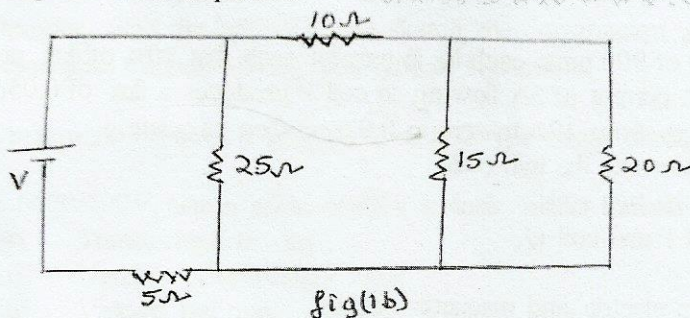
1.
 - a. State and explain Thevenin's theorem. (6)
 - b. In the circuit shown in fig (1b), find the value of supply voltage V , so that the 20Ω resistor can dissipate $180W$ of power. (6)



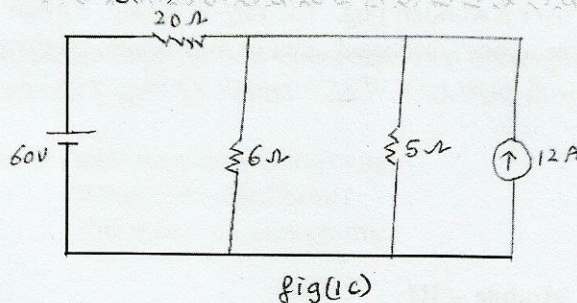- c. Using Norton's theorem, calculate the current flowing through the 6Ω resistor in the circuit shown in fig(1c) (8)



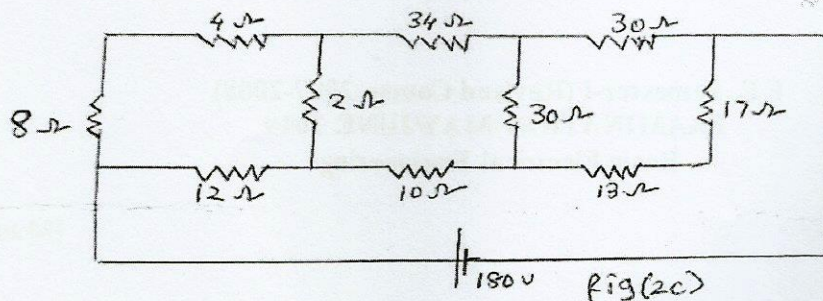2.
 - a. State and explain Kirchhoff's current law and Kirchhoff's voltage law. (6)
 - b. Define Resistance, inductance and Capacitance from their Circuit and Geometrical viewpoints. (6)
 - c. Find the current in the 10Ω resistor in the given network shown in fig(2c). (8)



fig(2c)

Module – II

3.
 - a. Explain the concept of mutually induced emf and self-induced emf. (7)
 - b. Derive expression for Force between two current carrying conductors. Comment on the direction of Force with respect to the direction of current in the conductors. (6)
 - c. Two identical coils P and Q of 900 turns each lie in parallel such that 70% of flux produced by one coil links to the other. A current of 5A flowing in coil P produces a flux of 0.05mwb in it. If the current in coil P changes from 12A to zero in 0.02sec, then calculate:
 - i) Mutual inductance between the two coils
 - ii) Self-inductances of the two coils.
 - iii) EMF induced in coil P and coil Q.
4.
 - a. Discuss the analogy between electric and magnetic circuits. (7)
 - b. Derive an expression for energy stored in magnetic circuit. (6)
 - c. A coil 120 turns is uniformly wound over a wooden ring. The ring is having a mean circumference of 400mm and a uniform cross – sectional area of 400sq. mm. A current of 5A is passed through the coil. Calculate:
 - (i) Magnetic field strength H
 - (ii) The flux density B
 - (iii) The total flux Φ .

Module – III

5.
 - a. Derive the expression for instantaneous current and instantaneous power in an AC circuit containing Resistance only. Draw neat and labeled waveforms and phasor diagram. (8)
 - b. A balanced star connected load of $(8+j6) \Omega$ is connected across three phase, 50Hz, 440V supply system. Calculate the line current, power absorbed and reactive volt – amperes. (6)
 - c. With a neat sketch explain how an alternating voltage is produced, when a coil is rotated in a magnetic field. Derive the expression for the instantaneous value of alternating sinusoidal emf. (6)

6.
 - a. Define the following terms as related to ac quantities: (6)
 - (i) Waveform
 - (ii) RMS value
 - (iii) Form factor
 - (iv) Frequency
 - (v) Active power
 - (vi) Power factor
 - b. In a Delta connected, three phase system, derive relationship between line voltage and phase voltage, line current and phase current and the expression for total power consumed. (8)
 - c. A coil dissipates 10W at 0.1 power factor lagging when connected to a 240V, 50Hz ac supply. Calculate the resistance, impedance and inductance of the coil. (6)

Module – IV

7.
 - a. Describe, with the help of a neat sketch, the construction and principle of operation of permanent magnet moving coil type of instrument. (10)
 - b. Distinguish between Core type and shell type single phase transformers. (5)
 - c. A 6600/400V, single phase 600KVA single phase transformer has 1200 primary turns. Find (5)
 - (i) Transformation ratio,
 - (ii) Number of secondary turns
 - (iii) Voltage per turn,
 - (iv) Secondary current when it supplies a load of 400KW at 0.8 power factor lagging.
8.
 - a. Derive the EMF equation of a single phase transformer. Mention the assumptions made. (6)
 - b. A balance 3-phase, star-connected load draws power from 440V supply. The two wattmeter's connected read 5KW and 1.2KW. Calculate power, power factor and current in circuit. (6)
 - c. Write short notes on the following: (8)
 - (i) Rating of a transformer
 - (ii) Efficiency of a transformer