

SEM 2 – 5 (RC 07-08)

F.E. Semester – II (RC 07-08) Examination, May/June 2018 BASIC ELECTRONICS ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :**
- 1) Attempt **any five** questions choosing at least **one** question from **each** Module.
 - 2) Draw **neat**, labelled diagrams **wherever** necessary.
 - 3) **All** symbols and abbreviations carry their usual meaning.
 - 4) Make **suitable** assumptions when **necessary**.

MODULE – I

1. a) Draw and explain the V-I characteristics of a silicon diode. Highlight the Forward-bias, Reverse-bias and No-bias regions on the graph. 6
b) Why are silicon diodes preferred over germanium diodes ? 2
c) Distinguish between avalanche and zener breakdown mechanisms in a semiconductor diode. 6
d) With neat diagrams explain the piecewise-linear and simplified equivalent circuits for a diode. 6
2. a) i) Determine the value of V_0 for the following network (Fig. 1)


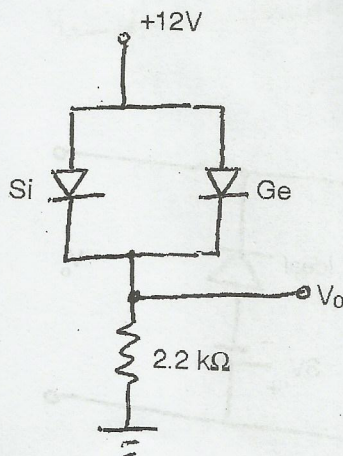


Fig. 1

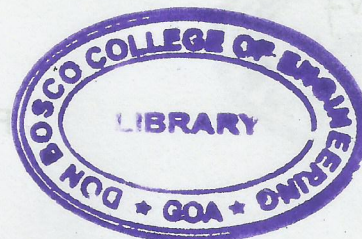

P.T.O.



- ii) Determine I_D , V_{D_2} and V_0 for the following circuit (Fig. 2).

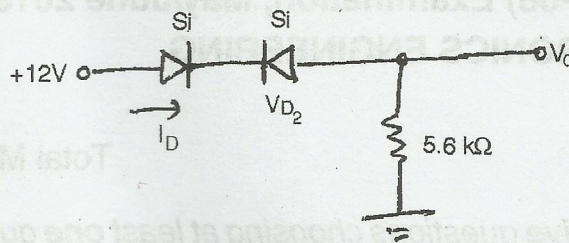


Fig. 2

- b) With a neat circuit diagram and waveforms explain the working of a full-wave bridge rectifier. Also draw the output waveform if a C-filter is connected across the load.
- c) For the following networks (Fig. 3) determine V_0 and draw the output waveform.

i)

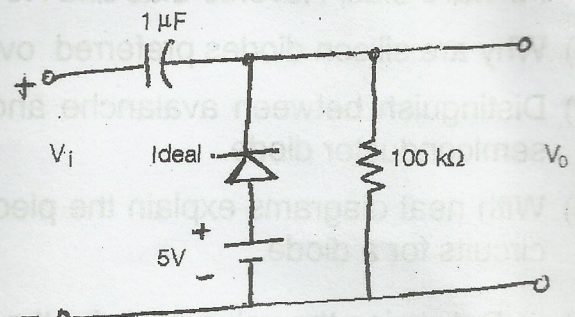
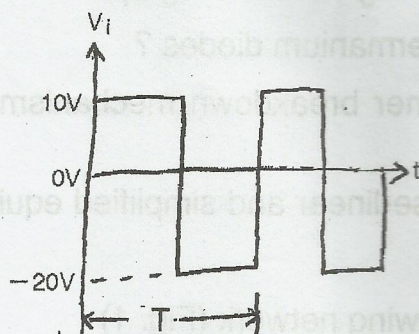


Fig. 3(a)

ii)



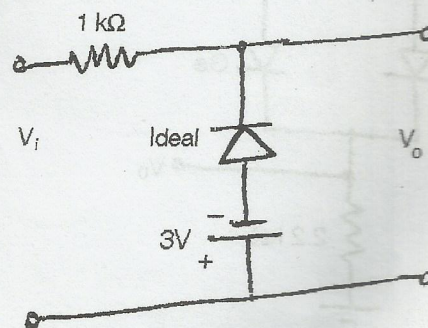
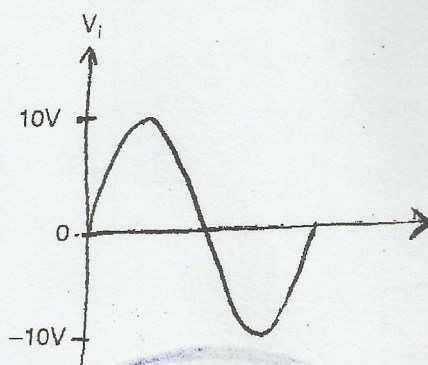


Fig. 3(b)

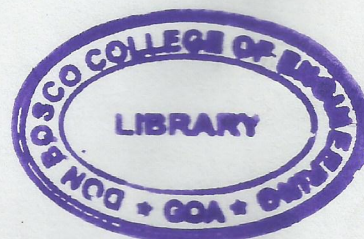

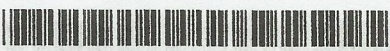

MODULE – II

3. a) Why is a transistor called a 'transistor' ? With a neat circuit-diagram, explain the amplifying action of a bipolar junction transistor.

6

b) With neat diagrams explain the common-emitter configuration of a bipolar junction transistor. Draw the collector and base characteristics (input and output characteristics). Explain the active, cut-off and saturation regions and highlight them on the graph.

8

c) Determine the following for the network given in Fig. 4

a) I_{BQ} and I_{CQ}

b) V_{CEQ}

c) V_B and V_C

d) V_{BC}

6



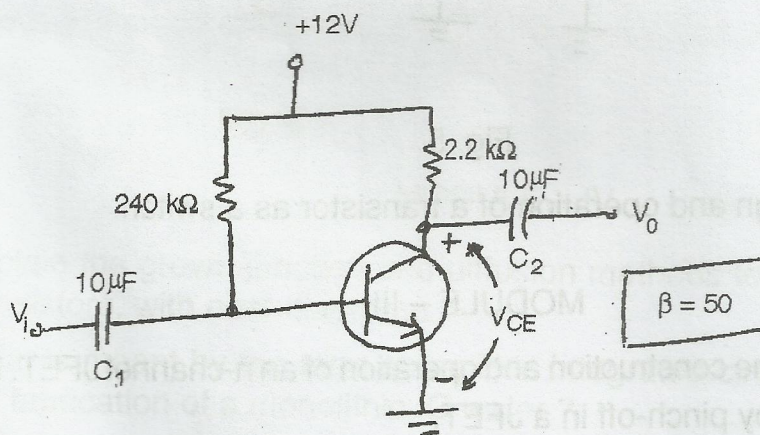


Fig. 4 Fixed bias circuit

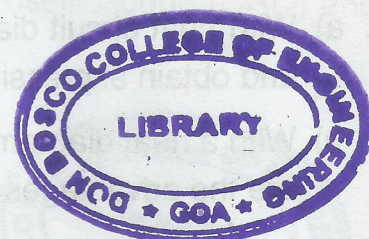

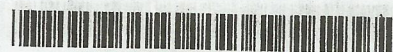

4. a) Draw the circuit diagram of an emitter-stabilized biased BJT circuit and hence derive the expressions for I_B , R_i , V_{CE} , V_C and V_B . What is the advantage of this circuit over fixed bias circuit ?
- b) Determine the dc bias voltage V_{CE} and the current I_C for the configuration shown in Fig. 5.

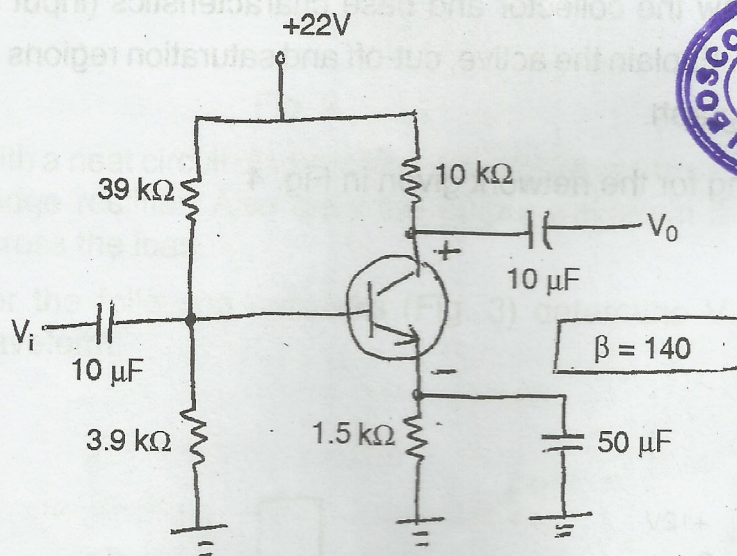


Fig. 5

- c) Explain the design and operation of a transistor as a switch.


MODULE – III

5. a) Explain in detail the construction and operation of an n-channel JFET. Explain what you mean by pinch-off in a JFET.
- b) Using the shorthand method, obtain the transfer curve for a JFET and sketch the transfer curve for a p-channel JFET with $I_{DSS} = 4 \text{ mA}$ and $V_p = 3 \text{ V}$.
- c) Explain the construction and basic operation of a n-channel depletion type MOSFET.
6. a) With neat circuit diagrams explain the analysis of a FET fixed bias circuit and obtain expressions for various voltages.
- b) With a neat diagram explain the construction and working of CMOS. What are the advantages of CMOS ?



c) Determine I_{DQ} , V_{GSQ} and V_{DS} for the network in Fig. 6.

8

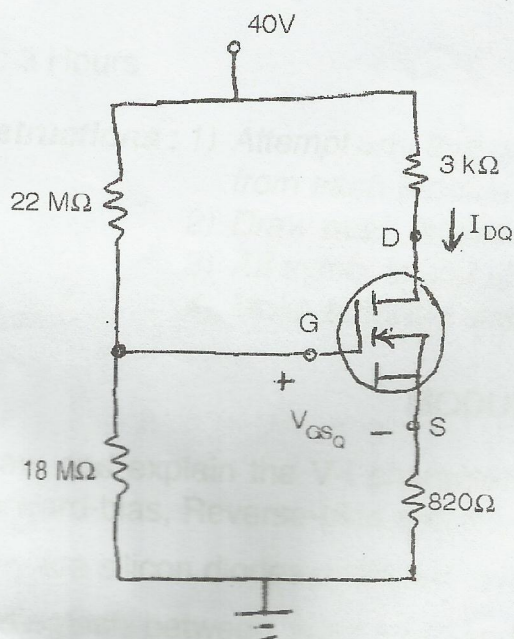

2N4351 (enhancement type)

$V_{GS} (Th) = 5V$

$I_D (on) = 3 mA$

at $V_{GS} (on) = 10V$

Fig. 6

MODULE – IV

7. a) Explain the grown-junction and diffusion methods to manufacture discrete transistors, with neat diagrams. 6
- b) What is meant by the term monolithic integrated circuit ? List the steps in the fabrication of a monolithic IC wafer ? 6
- c) Explain the op-amp operation in brief with differential input. 4
- d) Explain the concept of "feedback" and draw the block diagram of a basic feedback amplifier. 4
8. a) Explain the working of a reflective type field-effect LCD with a diagram. 6
- b) Draw the general block diagram of a cathode ray oscilloscope (CRO) and explain the operation of a CRO. 6
- c) Write short notes on (any two) : 8
- i) IR emitters and applications
 - ii) Solar cells
 - iii) Silicon Controlled Rectifier (SCR).

