

SEM 2 – 5 (RC 07 – 08)

F.E. (Semester – II) (RC) Examination, Nov./Dec. 2016
BASIC ELECTRONICS ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions:** 1) Attempt **any five** questions with atleast **one** question from **each** Module.
2) Assume suitable data **if necessary**.
3) **Neat** diagrams should be drawn **wherever** necessary.
4) Figures to the **right** indicate **full** marks.

MODULE – I

1. a) With the help of a neat diagram of a V/I characteristic, explain the working of a PN junction diode. Also explain the following terms :
i) Reverse saturation current
ii) Cut-in or knee voltage of the diode. 7
b) Differentiate between Zener and Avalanche breakdown. 3
c) Find V_o for the circuit. Given in Fig. 1 (c) 4

 


Fig. 1(c)

- d) With the help of neat diagram, explain the working of a Half Wave Voltage Doubler. Draw input and output voltage waveforms. 6
2. a) For the Zener diode network given in Fig. 2(a), determine V_L , V_R , I_Z , P_Z .
Given V_i is 16 V, R_L is 3 KΩ, V_Z is 10 V and P_{ZM} is 30 mW. 5

 


Fig 2(a)

P.T.O.



- b) The turns ratio of a transformer used in a half wave rectifier is $n_1 : n_2 = 10 : 1$. The primary is connected to the power mains : 220 V, 50 Hz. Assuming the diode resistance in forward bias to be zero, calculate :

- dc voltage across the load
- dc current through the load of $2.2 \text{ K}\Omega$
- PIV of the diode.

5

- c) Determine the output for the following circuit with the input waveform shown in Fig. 2(c).

5

 
 


Fig.2(c)

- d) Sketch the output waveform for the circuit shown in Fig. 2(d).

5


 


Fig.2(d)

MODULE – II

- Explain how CE configuration can be used as an amplifier. Also derive the expression for voltage and current gain of CE amplifier. 7
 - Draw CC transistor (pnp) configuration and explain why it is not used as a voltage amplifier. 3
 - Draw the circuit setup of CB (nnp) configuration and explain its output characteristics. 7
 - Explain why two back to back connected diodes cannot be used as a transistor. 3

 

4. a) For the biasing circuit shown in Fig. 4 (a) determine :

6

- | | | |
|-----------|-------------|------------|
| i) I_b | ii) V_c | iii) I_c |
| iv) V_e | v) V_{ce} | vi) V_b |

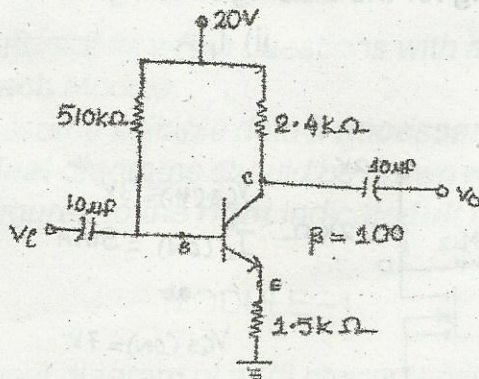


Fig.4(a)

b) Derive the stability factor $S(I_{CO})$ for Emitter stabilized bias circuit.

8

c) Explain the working of a transistor as a switch.

6

MODULE – III

5. a) With the help of neat diagram explain construction and operation of n channel JFET. Show the internal depletion regions and explain their shapes.

8

b) A P-channel JEFT has device parameter of $I_{DSS} = 9 \text{ mA}$ and $V_p = 5\text{V}$. Sketch the transfer characteristic.

4

c) Determine the following for the biasing circuit given in Fig. 5(c) :

8

- | | |
|---------------|--------------|
| i) V_{GSQ} | ii) I_{DQ} |
| iii) V_{DS} | iv) V_S |
| v) V_G | |

 


Fig.5(c)



6. a) With the help of neat sketches explain construction and output characteristic of n channel depletion type MOSFET. 8
- b) Write a short note on CMOS as an inverter. 6
- c) Determine the following for the biasing circuit given in Fig. 6(c). 8
- i) V_{GSQ} ii) I_{DQ}

 


Fig.6(c)

MODULE – IV

7. a) With a neat labelled diagrams explain the construction of a Silicon Controlled Rectifier and its working using the two transistor equivalent circuit. 6
- b) Describe the operation of a solar cell. 4
- c) Draw and explain Electron Gun Assembly in CRO. 6
- d) What is an op-amp ? Explain the single Ended input operation of an op-amp. 4
8. a) Give the manufacturing steps involved in the fabrication of diode in a Monolithic IC. 5
- b) Draw the general structure of a semiconductor IR Emitter diode and explain its working. 5
- c) Define Nyquist criterion. What is its significance ? 5
- d) Draw and explain the circuit of a Phase Shift Oscillator and write the expression for frequency of oscillation. 5