

Total No. of Printed Pages: 4

F. E. Semester –II (Revised Course 2016-17)

EXAMINATION OCTOBER 2020

Fundamentals Of Electronics And Telecommunication Engineering

[Duration : Two Hours]


[Total Marks : 60]

Instructions:

- 1) Answer THREE FULL QUESTIONS with ONE QUESTION FROM EACH PART.
- 2) Assume suitable data if necessary.
- 3) Figures to the right indicate full marks.

Part –A

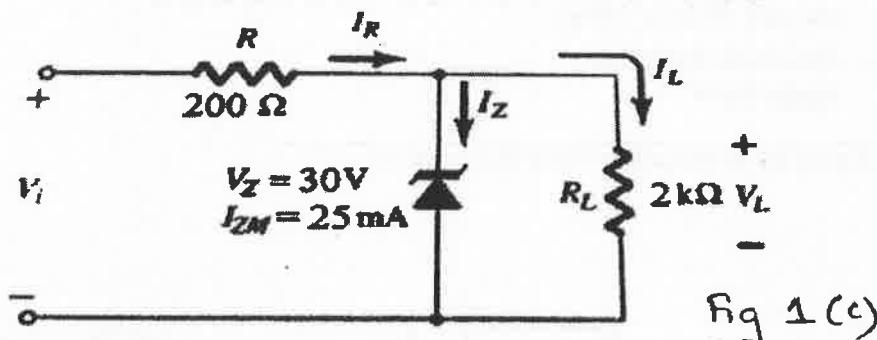1.
 - a) With the help of neat sketch explain forward biasing of PN junction diode. Also define knee voltage of a diode. 7
 - b) Differentiate between Avalanche and Zener breakdown. 3
 - c) Over what range of input voltage will the Zener circuit shown in figure 1(c) maintain 30 V across a 2k load, assuming that series resistance $R = 200\Omega$ and Zener current rating is 25 mA? 5



- d) Derive an expression for the output voltage (v_{dc}) and peak inverse voltage (PIV) of centre tapped full wave rectifier. 5
2.
 - a) With the help of a neat diagram explain the construction of N- channel JFET. Also draw the drain /output characteristics for the same. 7
 - b) Derive the relation between leakage currents of CB(I_{CBO}) and CE(I_{CEO}) configuration. 3
 - c) For the emitter- bias network shown in Fig2(c) ,determine: 5
 - (i) I_B
 - (ii) I_C
 - (iii) V_{CE}
 - (iv) V_C
 - (v) V_{BC}

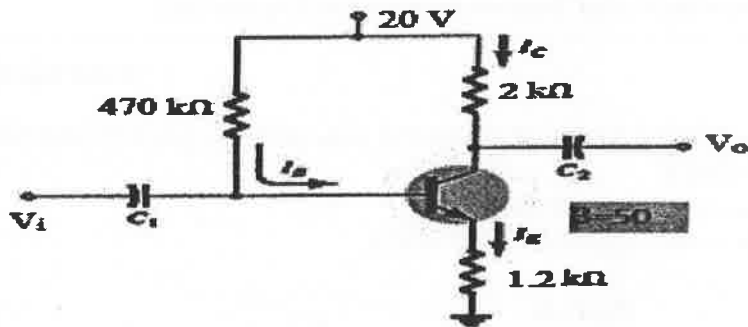


Fig 2(c)

d) With the help of neat diagram explain how Complementary MOSFET (CMOS) can be used as an inverter. 5

3. a) Explain different types of atomic bonds. 4
- b) In the bridge type circuit shown in Fig.3(b), the diodes are assumed to be ideal. Find: 6
- the d.c. output voltage
 - the peak inverse voltage
 - the output frequency
 - ripple factor.

Assume primary to secondary turns ratio to be 4:1

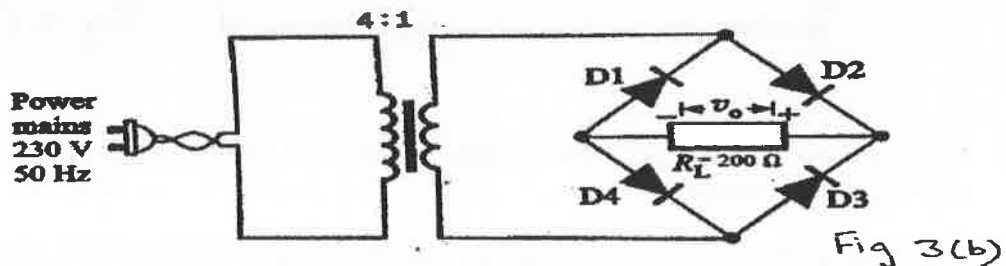


Fig 3(b)

- c) Why is the Fixed Bias Circuit not commonly used? 4
- d) With the help of a neat diagram explain the construction of N-channel Depletion MOSFET. 4
- e) What are the advantages of FET over BJT? 2

Part –B

4.
 - a) With the help of a two-transistor model, explain the working of a Silicon Controlled Rectifier. 5
 - b) Explain the following:
 - i) Common Mode Rejection Ratio(CMRR) 5
 - ii) Slew Rate 5
 - c) State the following Boolean Laws and prove them using the Truth Table method:
 - (i) Association Law
 - (ii) Absorption Law
 - d) Draw the Logic Symbols, construct Truth Tables, and with the help of circuit diagrams, explain the working of:
 - (i) AND 5
 - (ii) NOT

5.
 - a) Explain the working principle of Piezoresistive strain gauge. 4
 - b) What is PLC? How is it different from a computer? 4
 - c) Explain the following steps involved in the manufacturing of a single-sided Printed Circuit Board:
 - (i) Artwork Generation
 - (ii) Etching
 - (iii) Coating
 - d) Explain the need for modulation in a communication system with respect to the following:
 - (i) Multiplexing 6
 - (ii) Practicability of antennas
 - (iii) Narrowbanding

6.
 - a) With the help of a neat circuit diagram of an inverting amplifier using op-amp give the expression for its Closed Loop Voltage Gain. 3
 - b) Two square waves , A of 1 KHz and B of 2 KHz frequency are applied as input to the following Logic Gates. Draw the waveform in each case.
 - (i) AND Gate 2
 - (ii) XNOR Gate
 - c) With the help of logic diagrams , implement the following logic using NOR gate:
 - (i) AND Gate 5
 - (ii) OR Gate
 - (iii) NOT Gate
 - d) Differentiate between a microprocessor and microcontroller. 4
 - e) What are transducers? How can these be classified as modulating and self- generating transducers? Explain with the help of examples. 6

Part –C

- | | | |
|----|---|---|
| 7. | a) Explain N type semiconductor materials with the help of a neat diagram. | 5 |
| | b) With the help of a neat diagram explain how a BJT in Common Base (CB) configuration can be used as an amplifier. | 5 |
| | c) Draw the pin configuration of IC 741, and explain the use of each pin. | 5 |
| | d) With the help of neat sketches explain the construction, working and characteristics of LDR. | 5 |
| 8. | a) Draw and explain V-I characteristics of an ideal diode. | |
| | b) Why is Emitter Stabilized Bias Circuit an improvement over Fixed Bias Circuit? | 4 |
| | c) State the following Boolean Laws and prove them using the Truth Table method: | 6 |
| | (i) Commutative Law | 5 |
| | (ii) Distributive Law | |
| | d) With the help of a neat diagram explain the process of image transfer of artwork on to the board during the manufacture of a single –sided PCB | 5 |