



SEM 1 – 4 (RC 07-08)

F.E. (Semester – I) (RC 2007-08) Examination, Nov./Dec. 2018

BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours

Max. Marks : 100

- Instructions :** 1) Answer **any five** questions with **atleast one** question from **each** Module.
2) **Assume** suitable additional data if **necessary**.

MODULE – I

1. a) Define inductance and capacitance from their circuit, energy and geometrical viewpoints. 6
- b) State and explain Kirchhoff's laws. 6
- c) Find the Thevenin equivalent circuit between terminals A and B for the network shown in fig.(1c). Also calculate the current flowing through the 6.4Ω resistor. 8


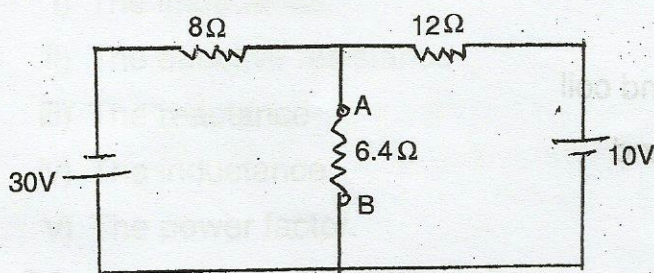


Fig. (1c)

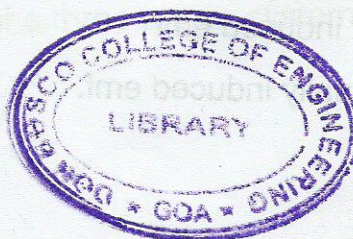2. a) State and explain Norton's theorem. 6
- b) Two resistances 20Ω and 40Ω are connected in parallel. A resistance of 10Ω is connected in series with the combination. A voltage of $200V$ is applied across the circuit. Draw the circuit. Find the current in each resistance and the voltage across 10Ω resistor. Find also the power consumed in all the resistances. 6



P.T.O.



- c) Find the current flowing through the galvanometer G, in the wheatstone bridge network shown in the fig (2c).

8

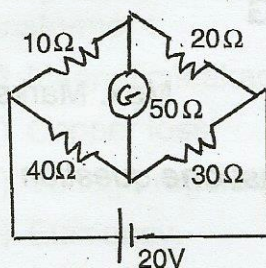


Fig (2c)

MODULE – II

3. a) State and explain Lenz's law. What are its applications. 6
- b) Derive an expression for coupling coefficient between two coils. 7
- c) An iron core has a mean cross-sectional area of 0.005 sq.m. and a mean circumference of 0.2m. The iron core has a relative permeability of 16000. It is wrapped with 300 turns of wire carrying 0.5 A of current. Calculate :
 - i) Reluctance of the core
 - ii) Inductance of the core and coil
 - iii) Magnetic field intensity and
 - iv) Magnetic flux density. 7
4. a) State the similarities and differences between electrical and magnetic circuits. 7
- b) Explain the following :
 - i) Magnetic potential
 - ii) Magnetic field strength
 - iii) Fleming's left hand rule.
 - iv) Faraday's laws
 - v) Self induced emf
 - vi) Mutually induced emf. 6



- c) The total inductance of two coils P and Q when connected in series is 0.5H or 0.2 H depending on the relative directions of the current in the coils. Coil P when isolated from coil Q, has a self inductance of 0.2 H. Calculate :
- i) The mutual inductance between the two coils
 - ii) The self inductance of coil Q.
 - iii) The coupling factor between the coils
 - iv) The two possible values of the induced emf in coil P, when the current is decreasing at 1000A/sec in the series circuit.

7

MODULE – III

5. a) Define phase difference. With neat waveforms, explain the concept of leading and lagging phase angle. Also define the term power factor.
- b) In a star connected, three phase system, derive the relationship between line voltage and phase voltage, line current and phase current and the expression for total power consumed.
- c) A series R-L circuit takes 10A and dissipates 1000W when connected to a supply of 250V, 50Hz. Calculate :
- i) The impedance
 - ii) The effective resistance
 - iii) The reactance
 - iv) The inductance
 - v) The power factor.

6

8

6

Draw the vector diagram.

6. a) Derive the expression for instantaneous current and instantaneous power in an AC circuit containing capacitance only. Draw neat and labeled waveforms and phasor diagram.
- b) A delta-connected load draws a current of 15A at a lagging power factor of 0.85 from a 400V, 50Hz, three-phase supply. Calculate :
- i) Resistance and inductance of each phase
 - ii) Power consumed.
- c) Graphically show the representation of a three phase system and explain the concept of phase sequence.

8

6

6



MODULE – IV

7. a) Briefly explain the following terms with respect to single phase transformer : 4
- i) Magnetic leakage
 - ii) Copper loss
 - iii) Voltage regulation
 - iv) Efficiency.
- b) Describe, with the help of a neat sketch, the construction and principle of operation of attraction type moving iron instrument. 10
- c) A 200KVA, 3300/240V, 50Hz single phase transformer has 80 turns on the secondary winding. Assuming an ideal transformer, calculate : 6
- i) Primary and secondary currents on full load
 - ii) The maximum value of flux
 - iii) The number of primary turns.
8. a) With the help of a neat phasor diagram, explain the working of a single phase transformer on no-load. 7
- b) Describe the open circuit and short circuit tests on a single phase transformer. 7
- c) The measurement of power in a 3-phase, star-connected load was done using two-wattmeter method. The load supplied was 30KW at 0.7 power factor lagging. Find the readings of each wattmeter. For what power factor will one of the wattmeters read zero ? 6