

SEM 1 – 4 (RC 07 – 08)

F.E. (Semester – I) (RC 2007-08) Examination, Nov./Dec. 2016

BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours


Total Marks : 100

- Instructions:** 1) Answer **any five** questions atleast **one** question from **each** Module.
2) **Assume** suitable data if necessary.

MODULE – I


1. a) Determine the voltage that must be applied at X – Y terminal such that voltage across 4Ω resistor is 5V.

7

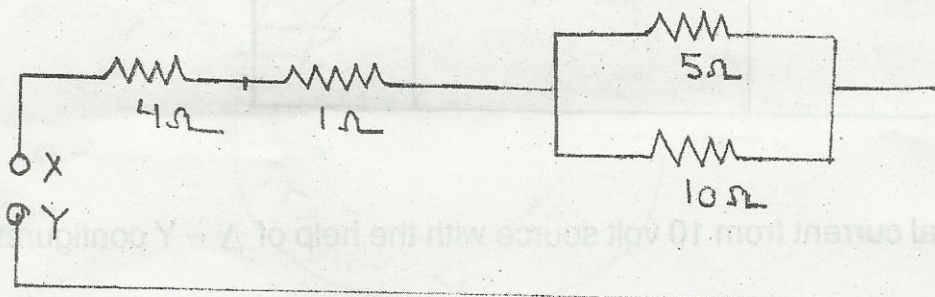

- b) Find the powerloss in the 1Ω resistor by using Thevenin's theorem for following circuit.

6

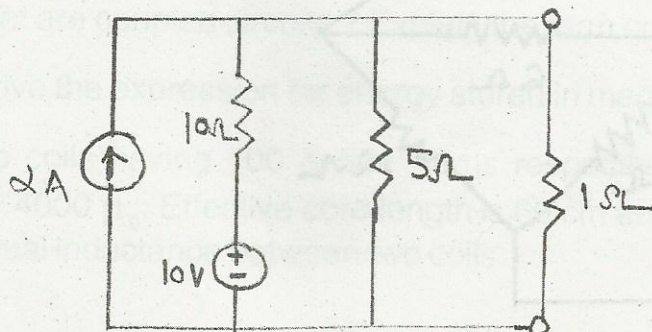




c) Find the equivalent inductance when three inductances are connected :

i) Series


ii) Parallel

2. a) State and prove maximum power transfer theorem for DC circuits.

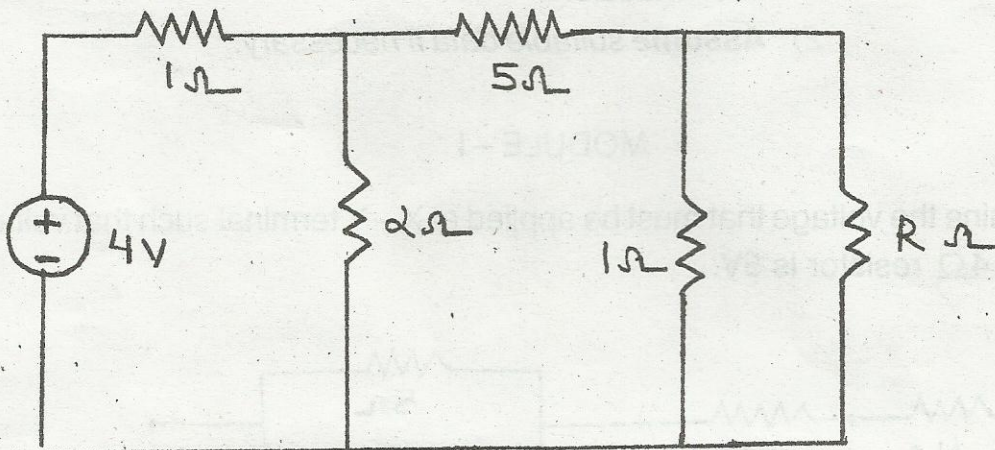b) Find the value of R in circuit such that maximum power transfer takes place. What is the amount of this power ?




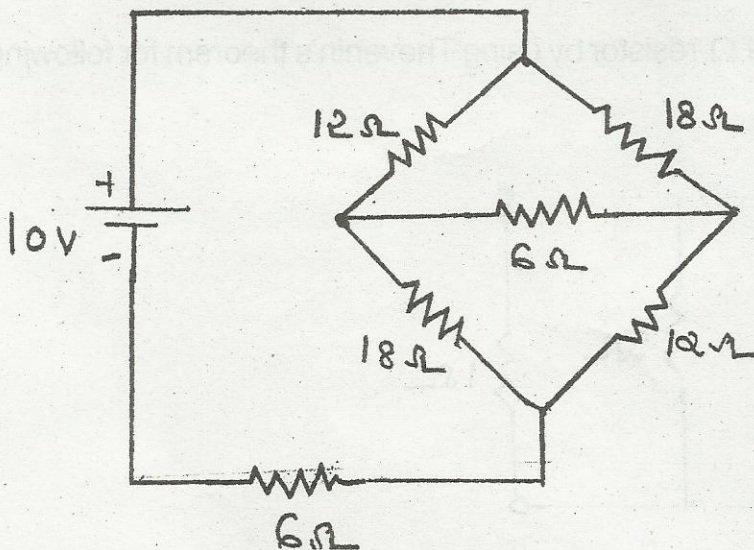c) Find the total current from 10 volt source with the help of $\Delta - Y$ configuration. 8




MODULE – II

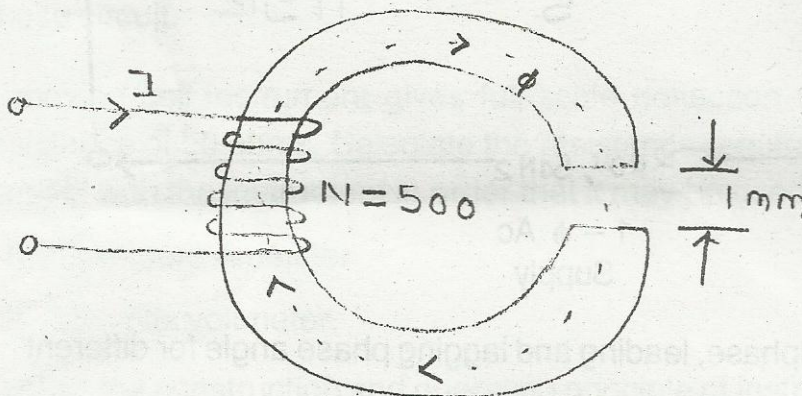3. a) Derive an expression for total MMF induced in series circuit with an airgap. 6
- b) State Amperes law, explain its significance and application. 6
- c) A wrought iron bar 30 cm long and 2 cm in diameter is bent into circular shape as shown in figure, an airgap of 1mm is cut across one of its limb. Area of cross section of core is $\pi \times 10^{-4} \text{ m}^2$. Calculate the excitation current of the coil, having 500 turns, to produce flux of 0.5 mwb. The relative permeability $\mu_r = 4000$. 8



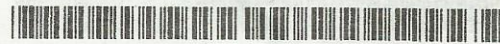
4. a) An electromagnet has an airgap of 4 mm and flux density in the gap is 1.3 wb/m^2 . Determine the ampere-turns for the gap. 4
- b) What are coupled circuits ? Explain the term coefficient of coupling. 6
- c) Derive the expression for energy stored in magnetic field. 6
- d) Two coils having 100 & 500 turns respectively are wound on core with $\mu = 4000 \mu_0$. Effective core length is 60 cm and core area is 9 cm^2 . Find mutual inductance between two coils. 4



MODULE – III

5. a) Determine the following for circuit.

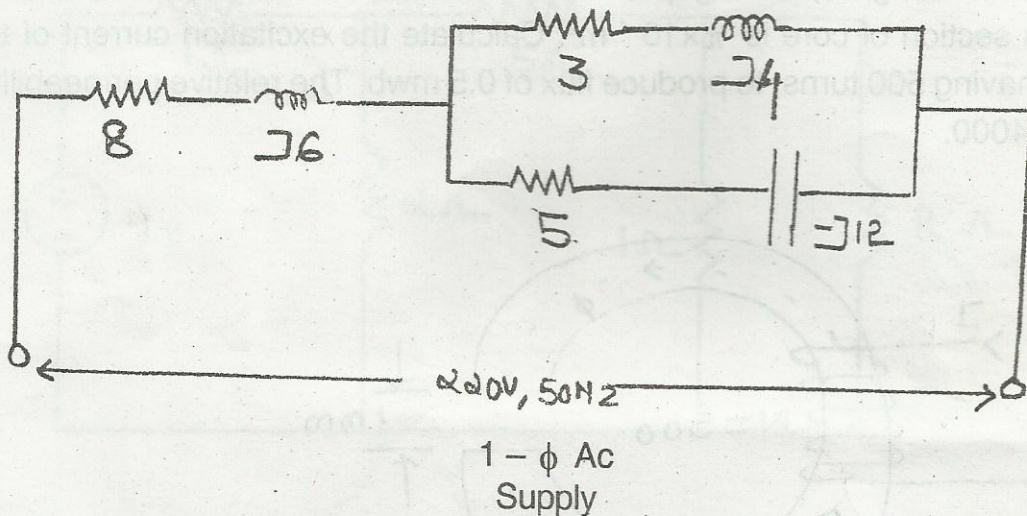- i) Total circuit current
- ii) Total active power
- iii) Power factor of circuit.



b) Explain concept of inphase, leading and lagging phase angle for different loads.

c) A three phase four wire 400 volts (L to L) system supplies a balanced star connected load having impedance of $20 \angle -30^\circ$ ohms in each phase. Find line currents. How much current is flowing through neutral.

6. a) Draw a phasor diagram showing following voltages $V_1 = 200 \sin 500t$, $V_2 = 300 \sin (500t + 45^\circ)$, $V_3 = 400 \cos 500t$. Find rms value of resultant voltage.

b) Derive relationship between current and voltage in a pure inductive and pure capacitive circuit. Draw the waveforms of instantaneous values of voltage and current.

c) Two impedances $Z_1 = 10 + j5$ and $Z_2 = 8 + j6$ are connected in parallel across voltage of $V = 200 + j0$. Calculate circuit current, power factor, reactive power, active power.



MODULE – IV

- a) A 500 KVA, 11000/400 V, 50 Hz, single phase transformer has 100 turns on the secondary winding calculate : 7
- i) Number of turns on prim wdg.
 - ii) Primary and secondary currents
 - iii) Maximum value of flux in core.
- b) Explain with equations how primary current changes, when load current is set up in the secondary winding of transformer. 6
- c) Explain the method of measurement of power for unbalanced load in three phase circuit. 7
3. a) A moving coil instrument gives full scale deflection with 10 mA and has resistance of 50 ohms. Calculate the resistance required to put in series/ parallel with the instrument in order that it may be used as : 6
- i) 10 Ampere Ammeter
 - ii) 100 volts voltmeter.
- b) Explain the construction and operating principle of instrument which can be used for measurement of Ac voltage. 6
- c) A single phase 3300/400 V transformer has following winding resistances and reactances $R_1 = 0.7 \Omega$, $R_2 = 0.011 \Omega$, $X_1 = 3.6 \Omega$, $X_2 = 0.45 \Omega$. The secondary is connected to load having resistance of 4.5Ω and inductive reactance of 3.2Ω . Calculate secondary terminal voltage and power consumed by the load. 8
-