



SEM 1 – 4

F.E. (Semester – I) (RC) Examination, Nov./Dec. 2013  
BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer **any five** questions with at least **one** question from **each** Module.  
2) Assume additional data **if necessary**.

MODULE – I

1. a) State and explain Norton's theorem. 6  
b) Using Kirchoff's laws find the current in the different resistances in the circuit given in fig. (1b). 7

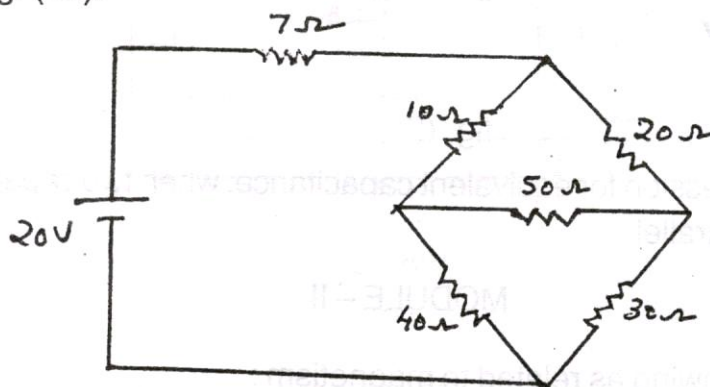


fig. (1b)

- c) Define inductance from its geometrical view point. Three inductors of inductance 10 H, 2.5 H and 2 H are connected in parallel. If the rate of change of current in 2 H inductor is 2A/s then find,  
i) Voltage across each inductor  
ii) Equivalent inductance  
iii) Total energy stored if the current in the coil is 4 A. 7
2. a) Define resistance from circuit, energy and geometrical view point. 6  
b) Using Thevenin's theorem find the current in the 6Ω resistance in the circuit given in fig. (2b). 6

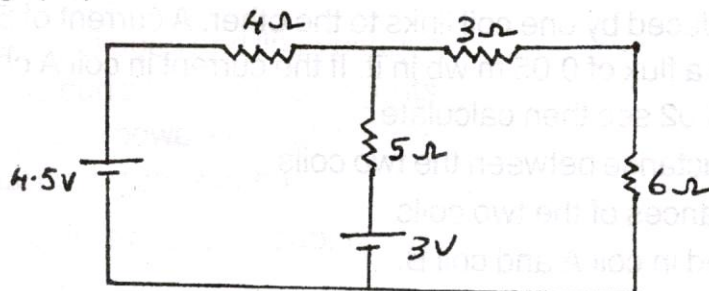


fig. (2b)

P.T.O.



- c) For the given current waveform, fig (2c), plot the voltage as a function of time in a resistance of  $10\Omega$ .

5

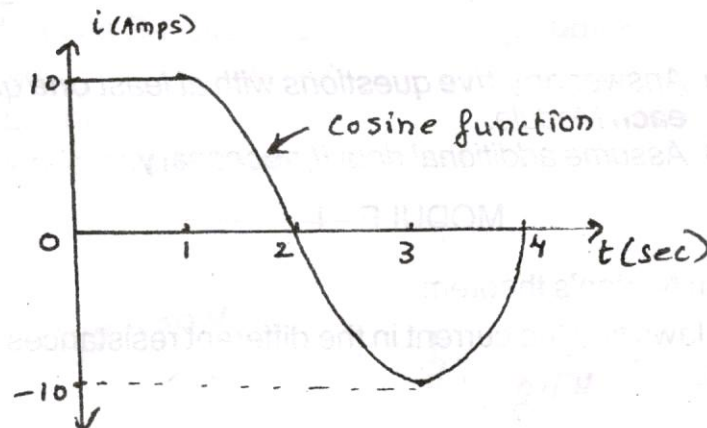


fig. (2c)

- d) Derive the expression for equivalent capacitance, when two capacitances are connected in parallel.

3

## MODULE – II

3. a) Explain the following as related to magnetism :

7

- i) Fleming's right hand rule
- ii) Ampere's law
- iii) Self inductance
- iv) Magnetically coupled coils
- v) Permeability
- vi) Reluctance
- vii) Magneto motive force.

- b) Discuss the analogy between electric and magnetic circuits.

6

- c) Two identical coils A and B of 1000 turns each lie in parallel planes such that 80% of flux produced by one coil links to the other. A current of 5A flowing in coil A produces a flux of 0.05 m wb in it. If the current in coil A changes from 12A to zero in 0.02 sec then calculate :

- i) Mutual inductance between the two coils
- ii) Self inductances of the two coils
- iii) Emf induced in coil A and coil B.

7



4. a) Derive the expression for coefficient of coupling between two magnetically coupled coils. 6
- b) Explain the concept of electromagnetic induction. Define : self inductance and mutual inductance. 6
- c) The magnetic circuit shown in fig. (4c) has a uniform cross-sectional area of  $4\text{cm}^2$  and relative permeability of 1200. If a coil of 1000 turns carrying current of 2 A is wound on central limb then, find flux in the different sections of the magnetic circuit. 8

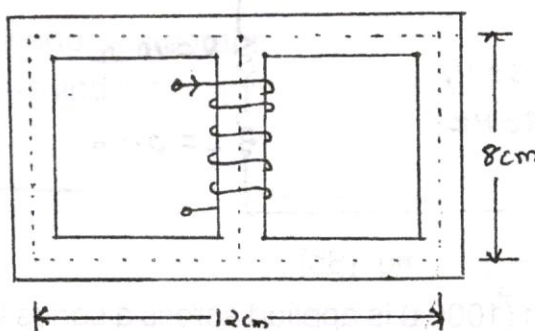


fig. 4(c)

## MODULE – III

5. a) Define the following terms as related to ac quantities : 5
- i) Phase angle
  - ii) Form factor of a sinusoidal current
  - iii) Frequency
  - iv) Apparent power
  - v) Power factor.
- b) Derive the expression for instantaneous current and instantaneous power in an ac circuit containing capacitance only. Draw neat and labelled waveforms and phasor diagram. 8
- c) A delta connected 3-phase balanced load  $(3 + j4)\ \Omega$  is connected across 230 V, 50 Hz supply. Find :
- i) Phase voltages and line voltages
  - ii) Phase currents and line currents
  - iii) Per phase power consumed
  - iv) Total power consumed.

The supply is 3-phase ac supply.

7





6. a) In a star connected, three phase system, derive the relation between line voltage and phase voltage, line current and phase current and the expression for total power consumed.

8

- b) For the given series R-L circuit, as shown in fig. (6b). Find :

- Impedance
- Circuit current
- Expression for total voltage and current.

5

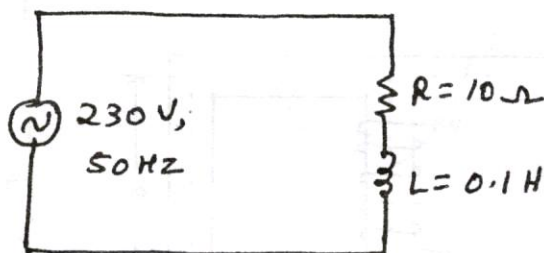


fig. (6b)

- c) A voltage  $e(t) = 150 \sin(1000t)$  is applied across a series RLC circuit where  $R = 40 \Omega$ ,  $L = 0.13H$ ,  $C = 10 \mu F$ .

7

- Compute the RMS value of current.
- Find the expression for instantaneous voltage across capacitor and inductor.

#### MODULE – IV

7. a) Describe the construction and working of moving iron instrument. Mention its advantages.

9

- b) Explain the two wattmeter method of power measurement in a 3-phase ac circuit.

6

- c) A Single phase 100 kVA, 440/220 V, 50 Hz transformer is operating at a maximum flux density of  $1.2 \text{ Wb/m}^2$  in the core. The effective cross-sectional area of the transformer core is  $180 \text{ cm}^2$ . Calculate the number of turns in the primary and secondary winding.

5

8. a) With the help of a neat phasor diagram, explain the working of a single phase transformer on no-load.

6

- b) Derive the emf equation in a single phase transformer.

6

- c) Write short notes on the following :

8

- Efficiency of a transformer
- Voltage regulation of a transformer.