

SEM 2-5 – (RC 07-08)

F.E. (Semester – II) (Revised in 2007-08) Examination, May/June 2017  
BASIC ELECTRONICS ENGINEERING


Duration : 3 Hours

Max. Marks : 100


**Instructions :** 1) Answer 5 questions choosing atleast one from each Module.  
2) Assume data if necessary.

MODULE – I

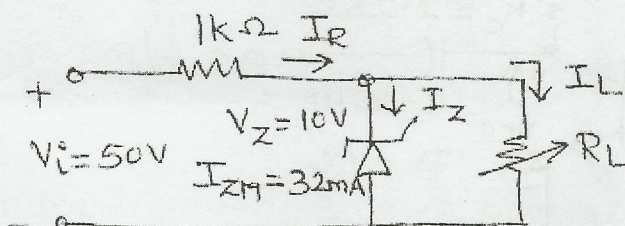1. a) Prove that the Ripple factor of a Full Wave Rectifier is 0.482. 4
- b) Explain the operation of a half wave Voltage doubler. 5
- c) Explain with circuit diagram the details of drawing loadline and determine the point of operation on the diode characteristics. 5
- d) Determine the range of  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10v. Determine the maximum wattage rating of the diode. 6



 2. a) The Positive Shunt Clipper shown in fig. below has the input waveform as indicated. Determine the values of  $V_{out}$  for each of the input alternations. 4



- b) Show that the maximum rectification efficiency of a half wave Rectifier is 40.6%. 6

P.T.O.






- c) Differentiate between Zener breakdown and Avalanche breakdown. 5
- d) Draw V-I characteristics of PN Junction diode and explain piecewise linear equivalent circuit of a diode. 5

## MODULE – II

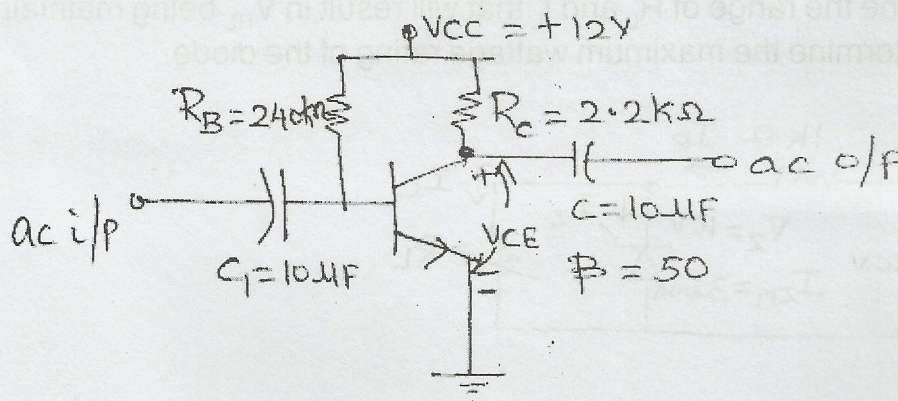3. a) Explain CE configuration of a NPN transistor. Draw the input and output characteristics. 5
- b) Explain how transistor can be used as an amplifier. 5
- c) With the help of necessary equations obtain the relation between  $\beta$  and  $\alpha$ . 4
- d) Determine the following for the fixed bias configuration of fig. 6
- i)  $I_{BQ}$  and  $I_{CQ}$       ii)  $V_{CEQ}$       iii)  $V_B$  and  $V_C$       iv)  $V_{BC}$




4. a) What do you mean by Stabilization of operating point ? Explain the reasons why Stabilization of Q point is necessary ? 5
- b) Transistor is connected in CE configuration in which collector supply is 8V and the voltage drop across resistance  $R_C$  in the collector circuit is 0.5V. The value of  $R_C = 800\Omega$ . If  $\alpha = 0.96$  determine
- i) Collector emitter voltage
- ii) Base current. 4
- c) Explain construction and various operating regions for a typical BJT. 6
- d) Compare the Biasing methods. Which is the best biasing technique ? Explain any one biasing technique. 5






MODULE – III

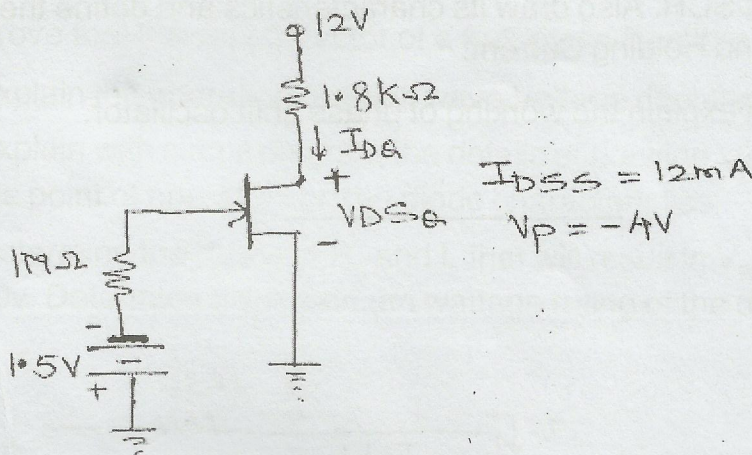5. a) With the help of neat diagram, explain the operation of P channel JFET. Also show internal depletion regions and explain their shapes. 8
- b) With the help of neat diagram and set of equations explain self bias configuration of JFET. 7
- c) For fixed bias configuration given below, determine the following : 5
- i)  $V_{GSQ}$       ii)  $I_{DQ}$       iii)  $V_{DS}$



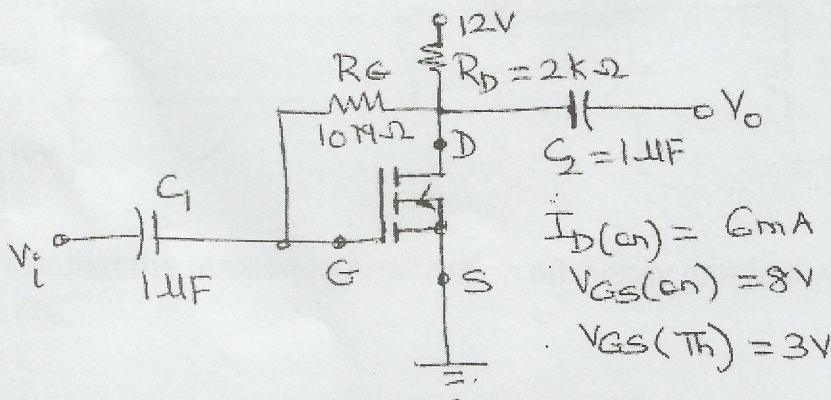6. a) Explain with a sketch why  $I_D$  exceeds beyond  $I_{DSS}$  if positive voltage is applied at the gate of n-channel depletion type MOSFET. 6
- b) With the help of neat sketches comment on the Polarity of various voltages and direction of current for n channel and P channel JFET. 6
- c) Determine  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DS}$  for Enhancement type MOSFET given below : 8







## MODULE – IV

7. a) Explain the block diagram of OPAMP. 4
- b) Give the manufacturing steps involved in Fabrication of discrete diode. 8
- c) With the help of neat diagram explain the working of transmissive type field effect LCD. 8
8. a) Explain how internal synchronization is achieved in CRO. 6
- b) Explain working of SCR. Also draw its characteristics and define the term Latching current and Holding Current. 8
- c) With neat diagram explain the working of phase shift oscillator. 6
-