

Total No. of Printed Pages:2

F.E. Semester –I (Revised Course 2019-20)
EXAMINATION FEBRUARY 2022
Basics of Electrical & Electronics Engineering

[Duration : Three Hours]

[Total Marks : 100]


Instructions:

- 1) Answer any two questions each from PART A and PART B and any one question from PART C.
- 2) Assume data wherever necessary

PART-A

- Q.1
- a) Differentiate between Renewable and non-Renewable energy resources (6)
 - b) Explain in brief the procedure for Nortonizing a circuit (8)
 - c) A coil of resistance $120\ \Omega$ is placed in magnetic field of 10^{-3}wb . The resistance of galvanometers is $400\ \Omega$ and coil has 100 turns. calculate the avg. emf and current if coil is moved $\frac{1}{10}$ sec from given field to a field of 0.2 mwb . (6)

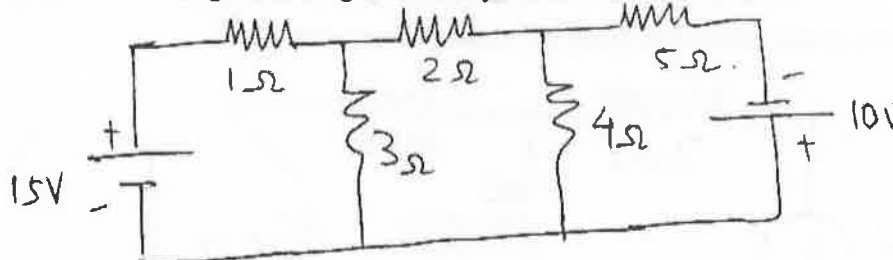- Q.2
- a) find current through $2\ \Omega$ using mesh analysis (8)




- b) Briefly explain the following terms with respect to single phase transformer (4)
 - i) magnetic leakage ii) Copper loss iii) voltage regulation iv) efficiency.
 - c) Derive expression for delta to star transformation (8)
- Q.3
- a) With respect to alternating current define the following term briefly. (6)
 - i) RMS value iv) Ripple factor
 - ii) peak Value v) frequency
 - iii) Average value vi) phase
 - b) with the help of power triangle explain the Concept of active power, Reactive power and apparent power with relevant equations (6)
 - c) Derive the relationship between line voltage and phase voltage in 3 phase star connected system. (8)

PART-B

- Q.4 a) Explain the construction and working principle of light emitting diode (LED). (6)
- b) 230 V AC supply is applied to a half wave rectifier through a transformer of ratio 10:1 find i) dc output voltage ii) PIV. Assume ideal diode (6)
- c) Explain in detail the working of zener diode in 3rd quadrant with relevant curve (8)
- Q.5 a) Explain the amplifying action of a Bipolar Junction transistor. (8)
- b) Differentiate between signal diode and Zener diode. (6)
- c) Describe the different breakdown mechanism in diodes (6)
- Q.6 a) Explain the fixed bias circuit for Bipolar Junction transistors. (8)
- b) Describe the construction and working of JFET (8)
- c) Differentiate between line regulation and load regulation for zener regulator (4)

PART-C

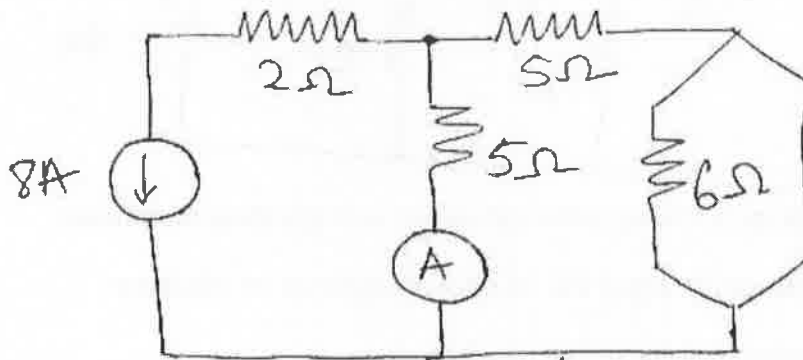- Q.7 a) for circuit given below determine the reading of ammeter. (6)



- b) Define the significance of iron loss and copper loss in transformer (6)
- c) Draw the block diagram of thermal power plant and explain its working. (8)
- Q.8 a) Derive the condition of maximum power transfer and also derive the equation of maximum power (10)
- b) Draw the VI characteristics of SCR and explain in detail various modes of operation (10)