



## SEM 1 – 4 (RC-07-08)

### F.E. (Semester – I) (RC 2007-08) Examination, May/June 2018 BASIC ELECTRICAL ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer **any five** questions, with atleast **one** from **each** Module.  
2) Assume additional data, if **necessary**.

#### MODULE – I

1. a) State and explain :

- Kirchoff's current law
- Kirchoff's voltage law.

6

b) In the circuit shown in fig. (1b), calculate the (i) total current (ii) current in  $5\Omega$  resistance (iii) power dissipated in  $6\Omega$  and  $7\Omega$  resistances.

6


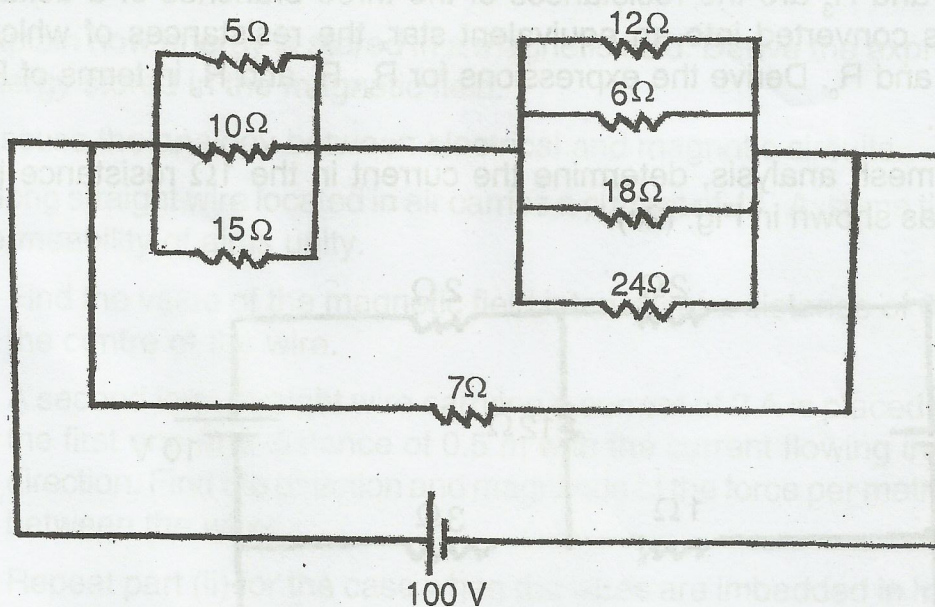


Fig. (1b)

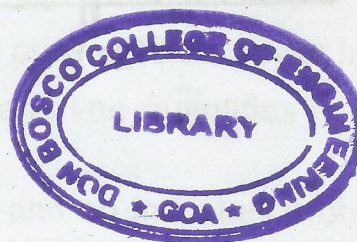

P.T.O.





- c) Using Thevenin's theorem, find the current in the  $6\Omega$  resistance in the circuit shown in fig (1c).

8


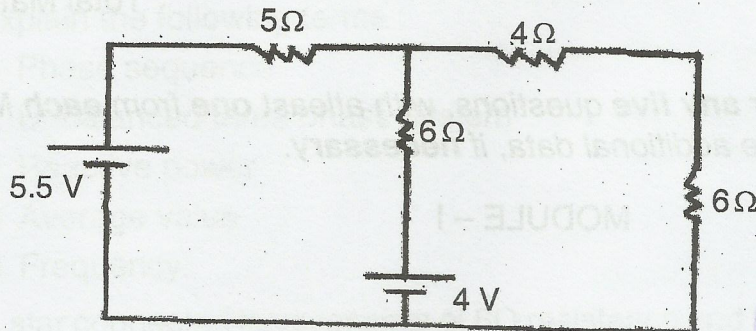


Fig. (1c)

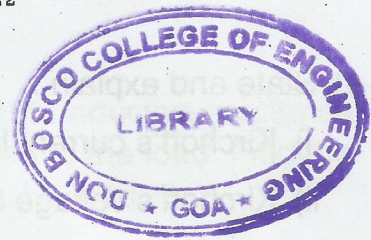

2. a) State and prove maximum power transfer theorem.

6

- b)  $R_1$ ,  $R_2$  and  $R_3$  are the resistances of the three branches of a delta. The delta is converted into an equivalent star, the resistances of which are  $R_a$ ,  $R_b$  and  $R_c$ . Derive the expressions for  $R_a$ ,  $R_b$  and  $R_c$  in terms of  $R_1$ ,  $R_2$  and  $R_3$ .

6

- c) Using mesh analysis, determine the current in the  $1\Omega$  resistance in the circuit as shown in Fig. (2c).

8

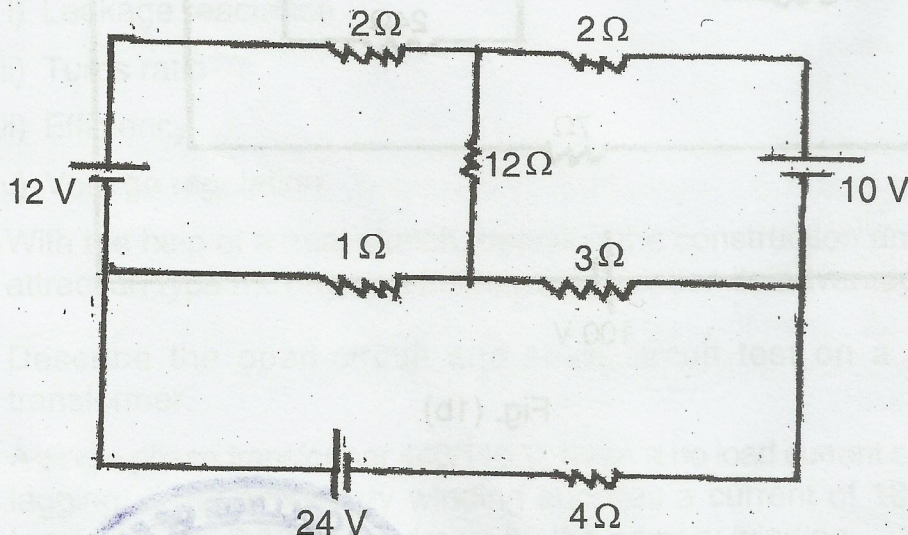



Fig. (2c)





MODULE – II

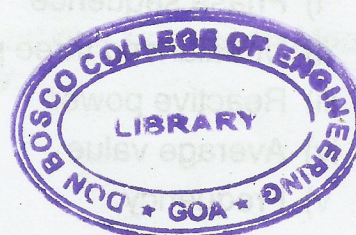3. a) Explain the concept of electromagnetic induction. 4
- b) Explain the following as related to magnetism : 4
- i) Magnetomotive force
  - ii) Self inductance
  - iii) Permeability
  - iv) Flemming's right hand rule.
- c) State and explain Ampere's law. 5
- d) Two magnetically coupled coils have a coefficient of coupling 0.85. When connected for series aiding, the total inductance is 100 mH and when connected for series opposing, the total inductance is 40 mH. Find the self inductance of both the coils and the mutual inductance between them. 7
4. a) Explain how energy is stored in a magnetic field. Derive the expression for energy stored in the magnetic field. 6
- b) Discuss the analogy between electrical and magnetic circuits. 7
- c) A long straight wire located in air carries a current of 4A. Assume the relative permeability of air is unity. 7
- i) Find the value of the magnetic field intensity at a distance of 0.5 m from the centre of the wire.
  - ii) A second long straight wire carrying a current of 2 A is placed parallel to the first one at a distance of 0.5 m with the current flowing in the same direction. Find the direction and magnitude of the force per metre, existing between the wires.
  - iii) Repeat part (ii) for the case when the wires are imbedded in iron having a relative permeability of 9,800 and a spacing of 0.05 m.



MODULE – III

5. a) Explain the concept of leading and lagging phase. Define power factor. 5
- b) Derive the relationship between phase and line quantities in a delta connected three phase system. 8
- c) A circuit consists of a resistance of  $20\Omega$  and an inductance of  $0.05\text{ H}$  connected in series. A supply of  $230\text{ V}$  at  $50\text{ Hz}$  is applied across the circuit. Find the current, power factor and power consumed by the circuit. 7





6. a) Show that, in a single phase R-circuit, the current is in phase with the applied voltage. Draw the phasor diagram and the waveforms of instantaneous values of voltage and current. 7
- b) Explain the following terms : 5
- i) Phase sequence
  - ii) Unbalanced three phase system
  - iii) Reactive power
  - iv) Average value
  - v) Frequency.
- c) A star connected load consists of  $6\Omega$  resistance and  $8\Omega$  inductive reactance in each phase. A supply of 440 V at 50 Hz is applied to the load. Find the line current, power factor and power consumed by the load. 4
- d) The expressions for instantaneous values of two voltages are given by  $V_1 = 12 \sin (\omega t - 40^\circ)$  and  $V_2 = 8 \sin (\omega t - 55^\circ)$ . Find the expression for the instantaneous value of resultant voltage by addition of the two voltages. 4

## MODULE – IV

7. a) Explain the working principle of a single phase transformer. 6
- b) Define the following terms related to single phase transformer : 4
- i) Leakage reactance
  - ii) Turns ratio
  - iii) Efficiency
  - iv) Voltage regulation
- c) With the help of a neat sketch, describe the construction and operation of attraction type moving iron instrument. Mention its advantages. 10
8. a) Describe the open-circuit and short circuit test on a single phase transformer. 7
- b) A single phase transformer 440/110 V, takes a no load current of 4A at 0.25 PF lagging. If the secondary winding supplies a current of 100 A at 0.9 PF lagging. Find the current drawn by the primary winding. 7
- c) A 3-phase, 400 V load takes an input of 40 kW at 0.45 PF lag. Find the reading of each of the two single phase wattmeters connected to measure the input. 6

