

Total No. of Printed Pages:3

**F.E. Semester II (Revised Course 2016-17)**  
**EXAMINATION FEBRUARY 2021**  
**Fundamentals of Electronics and Telecommunication Engineering**


[Duration : Two Hours]

[Total Marks :60]

- Instructions:-**
- 1) Answer THREE FULL QUESTIONS with ONE QUESTION FROM EACH PART.
  - 2) Assume suitable data **only if necessary**.
  - 3) All symbols, notations, and abbreviations have their usual meaning.


**PART A**

 1.
  - a) With neat diagrams compare insulators, semiconductors and conductors with respect to energy bands in solids. (6 mks)
  - b) Distinguish between Zener and avalanche breakdown mechanisms in a semiconductor diode. (6 mks)
  - c) Define and explain the following terms for a p-n junction diode:
    - i) Knee voltage, ii) reverse saturation current (4 mks)
  - d) Explain the mechanism which causes an LED to emit light. What factor determines whether visible light is emitted or not? (4 mks)
2.
  - a) i) Determine  $V_o$ ,  $I$  and  $I_D$  for the following circuit.



- ii) Determine  $V_o$  and  $I$  for the following circuit:

(6 mks)

 

- b) Derive the expression for the ripple factor of a full-wave bridge rectifier. Why is a bridge rectifier better than half-wave rectifier? (6 mks)
- c) i) Derive the expression for  $I_{dc}$ ,  $I_{rms}$  and  $V_{dc}$  for a half-wave rectifier.  
 ii) A half-wave rectifier is supplied with  $V_m = 20V$  from the transformer secondary, If  $R_L = 1k\Omega$ , calculate  $I_{dc}$  and PIV of each diode. (8 mks)
- 3 a) Derive the relationship between: i)  $\alpha$  &  $\beta$ , ii)  $I_{CEO}$  and  $I_{CBO}$  for a BJT. (6 mks)
- b) With the help of a circuit diagram explain the fixed bias circuit for a BJT, and derive the required equations. (6 mks)
- c) Explain with a neat diagram the working of a n-channel JFET. Draw the transfer characteristics. Show how the transfer curve is obtained. (8 mks)


### PART B

- 4 a) Two square waves of frequencies 100 Hz and 200 Hz are applied as inputs to the logic gates: i) NAND ii) XOR.  
 Draw the output waves for each case (4 mks)
- b) Compare positive and negative logic, in digital electronics. (4 mks)
- c) State and prove De Morgan's laws using a logic diagram and truth tables (6 mks)
- d) Draw the pin diagram for an op-amp. Explain the operation for a sinusoid input signal applied to the inverting terminal of an op-amp, and draw the output waveform. (6 mks)
5. a) What is an LVDT? With neat diagrams explain the internal construction and working principle of an LVDT. List two applications. (8 mks)
- b) Draw the basic block diagram of a PLC and explain its principle of working. (6 mks)
- c) With the help of a neat diagram explain the components of a basic communication system. (6 mks)

6. a) Why is a NAND gate called a “universal logic gate”? Using logic diagrams, implement the following logic gates using only NAND gates: i) XOR ii) OR (5 mks)
- b) Why is modulation needed in communication systems? With the help of a diagram, explain the basic concept of amplitude modulation. (6 mks)
- c) What is a strain gauge? Define “gauge factor” of a strain gauge and write the expression for it. What is its significance? (6 mks)
- d) Reduce the following Boolean expression and implement the simplified expression using logic gates:  $Y = \bar{A}\bar{B} + A\bar{B}$ . Verify using a truth table. (3 mks)
 
### PART C

- 7 a) Draw the block diagram of a microcontroller and list two applications. How is it different from a microprocessor? (5 mks)
- b) State the associative and distributive laws of Boolean algebra, and prove them using truth tables (6 mks)
- c) Draw waveforms for the modulating and modulated signals for FM, and define modulation index for the same. (4 mks)
- d) Give the steps involved in the manufacture of a single sided PCB with the help of a flow diagram. (5 mks)
- 8 a) For the Zener regulator circuit shown below, determine the range of  $R_L$  that shall result in the load voltage being maintained at 10 V. (6 mks)



- b) Simplify the following expressions using laws of Boolean algebra: (6 mks)
- i)  $Y = ABC + \bar{B}\bar{C}D + \bar{A}BC$
- ii)  $Y = \bar{A}BC\bar{D} + BC\bar{D} + B\bar{C}\bar{D} + B\bar{C}D$
- c) Draw the output characteristics for a BJT npn transistor amplifier in common emitter configuration and explain the various regions. (8 mks)

