

## SEM 1-4 (RC 2016-17)

# F.E. Semester – I (RC 2016-17) Examination, Nov./Dec. 2016 FUNDAMENTALS OF ELECTRICAL ENGINEERING (New)


Duration: 3 Hours Total Marks: 100

Instructions: 1) Answer any two questions from Part - A.

- 2) Answer any two questions from Part B.
- 3) Answer any one question from Part C.
- 4) Assume suitable data, if required.

#### PART-A

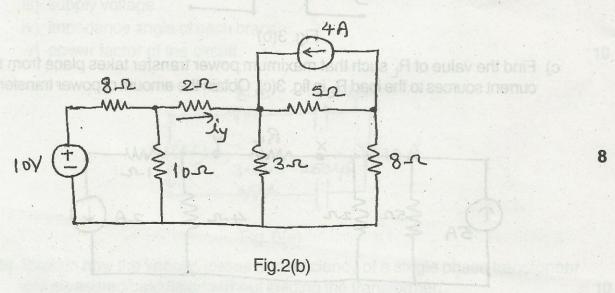- 1. a) Explain with the help of schematic/Block diagram the working of a thermal power plant.
  - b) Draw a single line diagram representing electrical power system. Write typical values of voltages at different levels.
  - c) When one coil of a magnetically coupled pair has a current 5A the resulting fluxes  $\phi_{11}$  and  $\phi_{12}$  are 0.2 mWb and 0.4mWb, respectively. If the turns are 500 and 1500, find  $L_1$ ,  $L_2$ , M and coefficient of coupling K.
- 2. a) Define the following terms:
  - i) Ideal and practical current source
  - ii) Planar circuits.
  - b) Using superposition theorem find the current i<sub>v</sub> in the circuit of fig. 2(b)



8

7

5

4

8

8

c) The venize the bridge circuit across a - b in fig. 2(c).



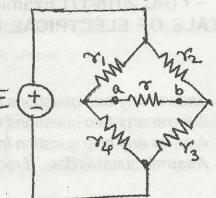


Fig.2(c)

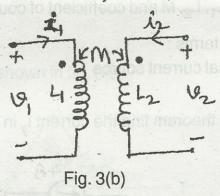- 3. a) State and explain Norton's theorem.
  - b) In the fig. 3(b), let  $L_1 = 0.4$  H;  $L_2 = 2.5$  H; K = 0.6 and  $i_1 = 4$ ,  $i_2 = 20$  cos (500 t 20°) mA. Evaluate the following quantities at t = 0.
    - 1) i2
    - 2) V<sub>1</sub>
    - 3) The total energy stored in the system.



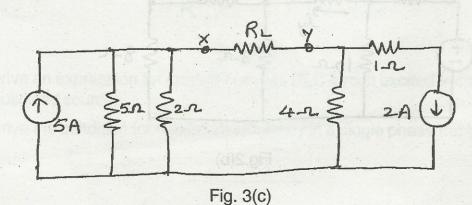c) Find the value of  $R_L$  such that maximum power transfer takes place from the current sources to the load  $R_L$  in fig. 3(c). Obtain the amount of power transfer.



8

4

8

6

6

8

10

10



### PART-B

- 4. a) Define the following terms:
  - i) Average value
  - ii) Form factor
  - iii) Active power
  - iv) Power factor.
  - b) A 4 ohm resistor is connected to a 10 mH inductor a 100 V, 50Hz voltage source. Find
    - i) Power factor of the circuit
    - ii) Total power supplied.
  - c) A  $10\Omega$  resistor is connected in parallel with a  $100\,\mu$ F capacitor. Supply being 5A, 50 Hz current source, find the rms and instantaneous branch currents through the capacitor and resistor.
- 5. a) Is three phase system preferred over single phase system? Why?
  - b) Explain the working of a single phase transformer.
  - c) Three similar coils, each having a resistance of  $3\Omega$  and an inductive reactance of  $4\Omega$  are connected in i) Y and ii)  $\Delta$ , across a 400 V, three-phase supply. Calculate for each connection the readings on each of the two wattmeters connected to measure the power by the two-wattmeters method.
- 6. a) In the circuit shown in fig. 6(a) if the supply frequency is 60 Hz, find :
  - i) drop across each circuit element
  - ii) total resistive and capacitive drop
  - iii) supply voltage
  - iv) impedance angle of each branch
  - v) power factor of the circuit.

8-2 8004F V(AC) 3.52 2504F V 10 A

Fig. 6(a)

 Explain how the various losses and efficiency of a single phase transformer are measured/calculated without loading the transformer.

5

6

4

5

6

5

#### PART-C

- 7. a) Differentiate between conventional and non conventional sources of energy. 5
  - b) Find current I in the network shown in fig. 7(b).

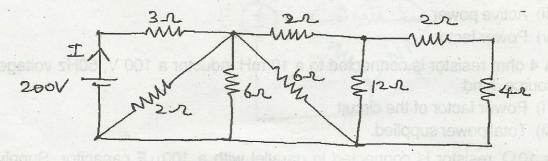


Fig. 7(b)

- c) A coil takes current of 160° A (lag) from 100 V, 60 Hz, supply. Calculate its inductances, resistance and impedance.
- d) Draw the equivalent circuit of a transformer.
- 8. a) Define the following terms:
  - i) Reluctance
  - ii) Ampere's law.
  - b) Find R<sub>xy</sub> in the circuit shown in fig. 8(b)

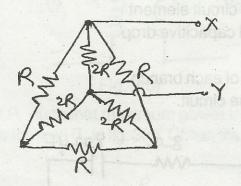


Fig. 8(b)

- Derive an expression for current in series RLC-circuit excited from a sinusoided source.
- d) Derive the condition for maximum efficiency in a single phase transformer.