

Total No. of Printed Pages:3

F.E. Semester-II (Revised Course 2007-2008)
EXAMINATION MAY/JUNE 2019
Basic Electronic Engineering

[Duration : Three Hours]


[Max. Marks : 100]

Instructions:

1. Attempt any five questions choosing at least one question from each module.
2. Assume suitable data only if necessary.

Module I

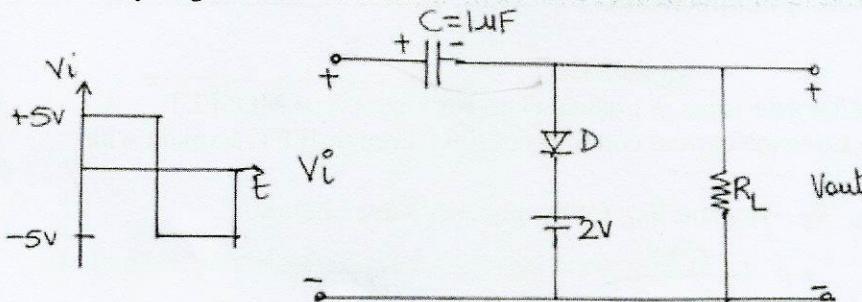- Q.1
- a) Explain Load line analysis and find the point of operation on the diode characteristics. 06
 - b) Show that the maximum Rectification Efficiency of a Half wave Rectifier is 40.6%. 10
 - c) Sketch the output waveform for the circuit show in fig below assuming RC time constant is very large and diode is ideal. 04




- Q.2
- a) Explain the following terms i) Transition Capacitance ii) Diffusion capacitance 04
 - b) In a center tap full wave rectifier $R_L = 1 \text{ K}\Omega$ and each diode has a forward biased dynamic resistance $r_f = 10 \Omega$. The voltage across each half of the secondary winding is $220\sin\omega t$. Determine I_m , I_{dc} , I_{rms} and ripple factor. 05
 - c) Explain why it is necessary to use a voltage regulator circuit in the power supply. 06
 - d) Draw V-I characteristics of PN junction diode. Explain Piecewise linear equivalent circuit of a diode. 05

Module II

- Q.3
- a) What is the need for biasing a transistor. Explain any one technique of transistor biasing. 08
 - b) Draw the circuit setup of Common base (NPN) transistor configuration and explain how its input and output characteristics are plotted. 08
 - c) What do you mean by stabilization of operating point? Explain the reasons why stabilization of Q point is necessary. 04

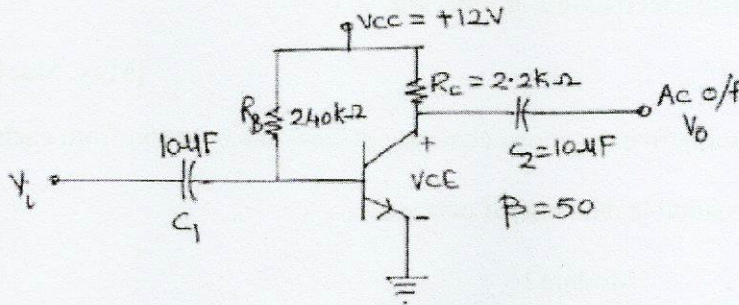
- Q.4 a) Determine the following for the network given in fig a) I_{BQ} and I_{CQ} b) V_{CEQ} c) V_B and V_C d) V_{BC} 06




- b) Explain the amplifying action of Bipolar junction Transistor. 05
c) Draw the circuit setup and explain how the static input characteristics of a CE transistor are plotted. 05
d) Explain Fixed bias BJT biasing configuration. 04

Module III

 - Q.5 a) Draw and explain Drain Characteristics of n-channel enhancement type MOSFET 06
b) Even after Pinch off Condition the current continues to flow through JFET. Explain with relevant diagrams. 06
c) Determine I_{DQ} , V_{GSQ} , V_D , V_S , V_{DS} and V_{DG} for the network shown below. 08



- Q.6 a) Explain the operation of an N-channel JFET. Show the internal depletion regions and explain their shape. 08
b) Explain with the help of diagram the basic CMOS operation. 06
c) Determine the following for the network shown in fig below i) V_{GSQ} ii) I_{DQ} iii) V_{DS} 06
iv) V_D v) V_G vi) V_S

 


Module IV

- a) Write short notes on (Any two)
- Solar cell
 - IR emitter
 - Thermistor
- b) Design a monolithic IC to implement the following schematic

08

06

 

- c) Explain with block diagram the trigger operation of CRO.

06

Q.8

- Draw and explain Internal block diagram of OP-AMP
- Explain the working of SCR using two transistor equivalent circuit.
- Draw and explain the working of Reflective type field effect LCD.
- Draw and explain Electron gun assembly used in CRO

05

05

06

04