



## SEM 2 – 5 (RC 07-08)

F.E. (Semester – II) (RC 2007-08) Examination, Nov./Dec. 2018  
BASIC ELECTRONICS ENGINEERING

Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Attempt **any five** questions choosing at least **one** from **each** Module.  
2) Draw **neat**, labelled diagrams **wherever** necessary.  
3) **All** symbols and abbreviations carry their **usual** meaning.  
4) Make **suitable** assumptions when **necessary**.

### MODULE – I

1. a) Draw and explain the V-I characteristics of a silicon diode. Highlight the forward -bias, reverse-bias and no-bias regions on the graph. 6  
b) Differentiate between transition and diffusion capacitance in a p-n junction diode. 4  
c) With neat diagrams explain the piecewise linear and simplified equivalent circuits for a diode. 6  
d) Explain the avalanche-breakdown mechanism in a p-n junction diode. 4
2. a) i) Determine the value of  $V_o$  for the following network (Fig. 1)


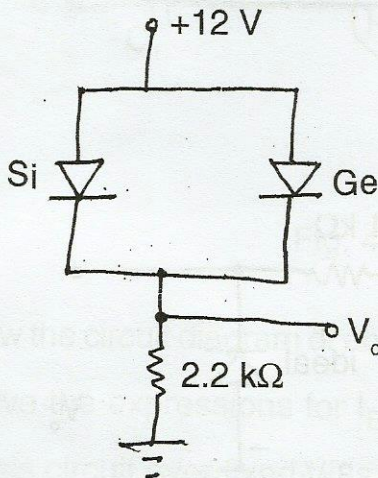


Fig. 1

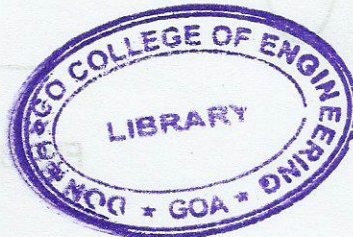

P.T.O.





- ii) Determine  $I_D$ ,  $V_{D_2}$  and  $V_o$  for the following circuit. (Fig. 2)

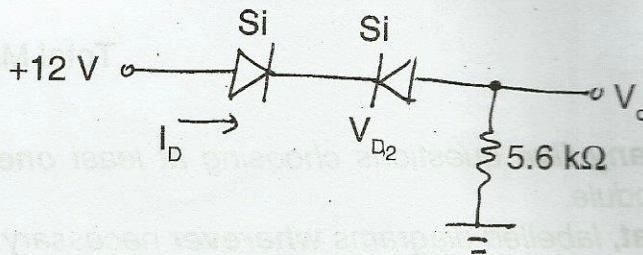


Fig. 2

- b) With a neat circuit diagram and waveforms explain the operation of a full-wave center-tap rectifier. Also draw the output waveform if a C-filter is connected across the load. What is the PIV of each diode ?
- c) For the following networks (Fig. 3) determine  $V_o$  and draw the output waveform.

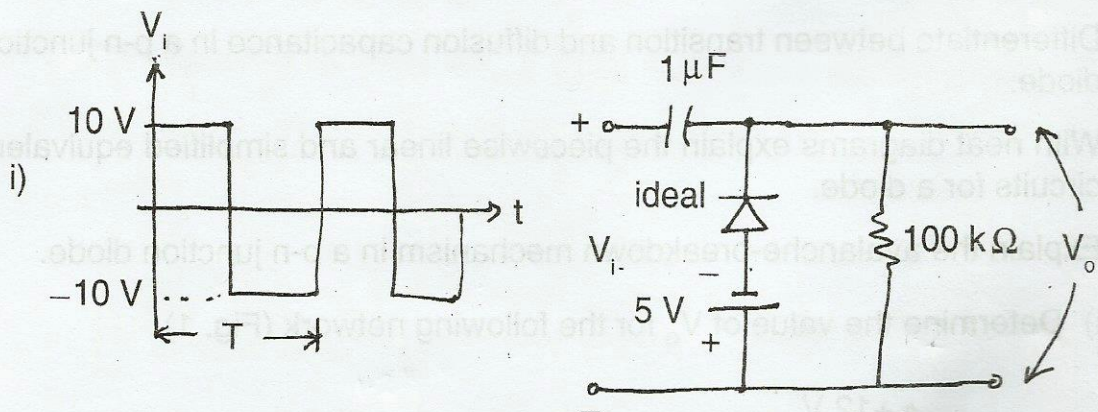


Fig 3 a)

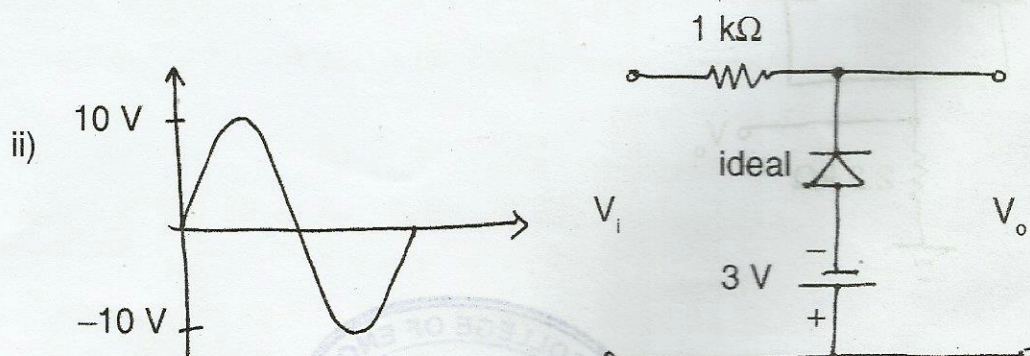


Fig. 3b)





MODULE – II

3. a) Why is a transistor called a 'transistor'? With a neat circuit diagram, explain the amplifying action of a bipolar junction transistor.

6

- b) With neat diagrams explain the common-emitter configuration of a bipolar junction transistor. Draw the collector and base (input and output) characteristics. Explain the active, cut-off and saturation regions and highlight them on the graph.

8

- c) Determine the following for the network given in Fig. 4.

6

a)  $I_{BQ}$  and  $I_{CQ}$

b)  $V_{CEQ}$

c)  $V_B$  and  $V_C$

d)  $V_{BC}$

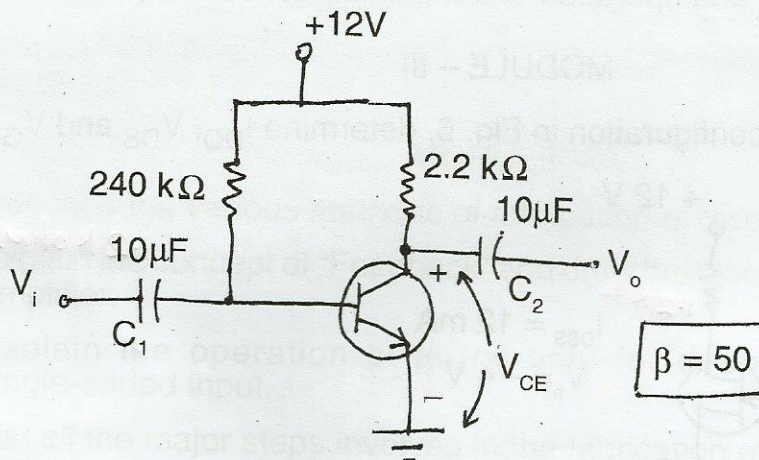


Fig. 4 : Fixed bias circuit

4. a) Draw the circuit diagram of an emitter-stabilized biased BJT circuit and hence derive the expressions for  $I_B$ ,  $R_i$ ,  $V_{CE}$ ,  $V_C$  and  $V_B$ . What is the advantage of this circuit over fixed-bias circuit?

7





- b) Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for the configuration shown in Fig. 5.

8

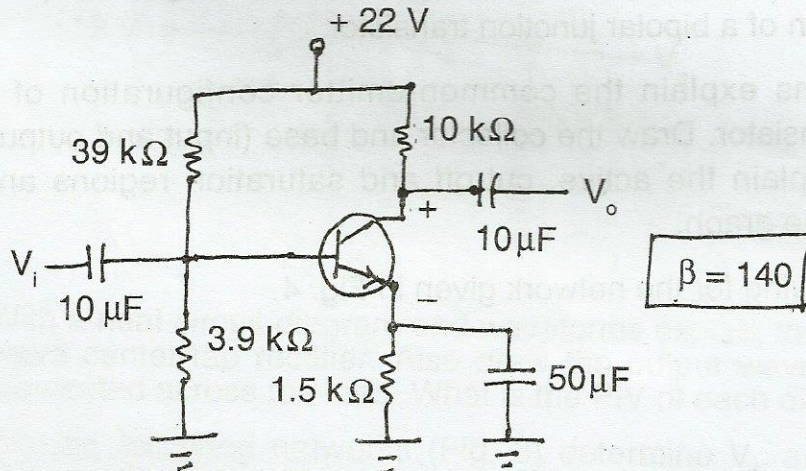


Fig. 5

- c) Explain the design and operation of a transistor as a switch.

5

## MODULE – III

5. a) For the fixed bias configuration in Fig. 6, determine  $I_{DQ}$ ,  $V_{DS}$  and  $V_{GSQ}$ .

6

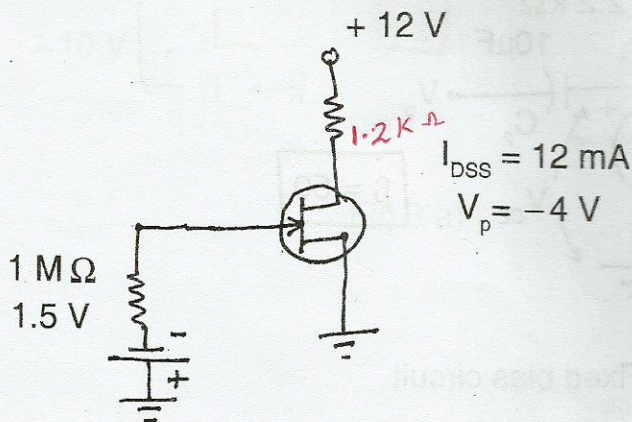


Fig. 6

- b) Explain the construction and operation of an n-channel depletion type MOSFET. Also draw output and transfer characteristics of the same.
- c) With the help of a neat diagram and set of equations explain the self-bias circuit of a JFET.

8


6





6. a) Determine  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_{DS}$  for the network shown below : (Fig. 7)

8

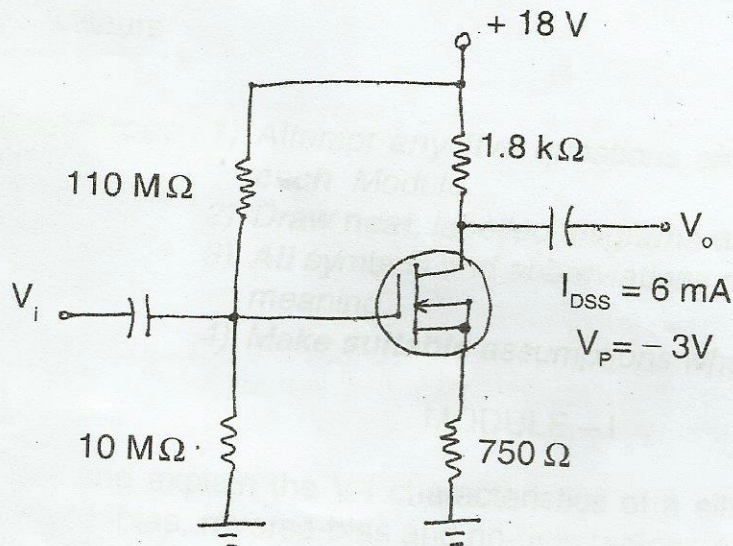

- b) Write a short note on CMOS as an inverter.  
c) Explain the construction and working of p-channel enhancement-type MOSFET.

6

6

#### MODULE – IV

7. a) Describe the various methods of fabrication of discrete diodes.  
b) Explain the concept of "Feedback" and draw the block diagram of a feedback amplifier.  
c) Explain the operation of an op-amp for double-ended output with single-ended input.  
d) List all the major steps involved in the fabrication of a monolithic IC wafer.
8. a) Explain the working of a transmissive type field-effect LCD with a diagram.  
b) Draw the symbol for an SCR and explain its working with a diagram.  
c) Write short notes on **(any two)** :  
i) Photodiodes and applications  
ii) Solar cells and applications  
iii) IR emitters and applications.

6

4

6

4

6

6

8